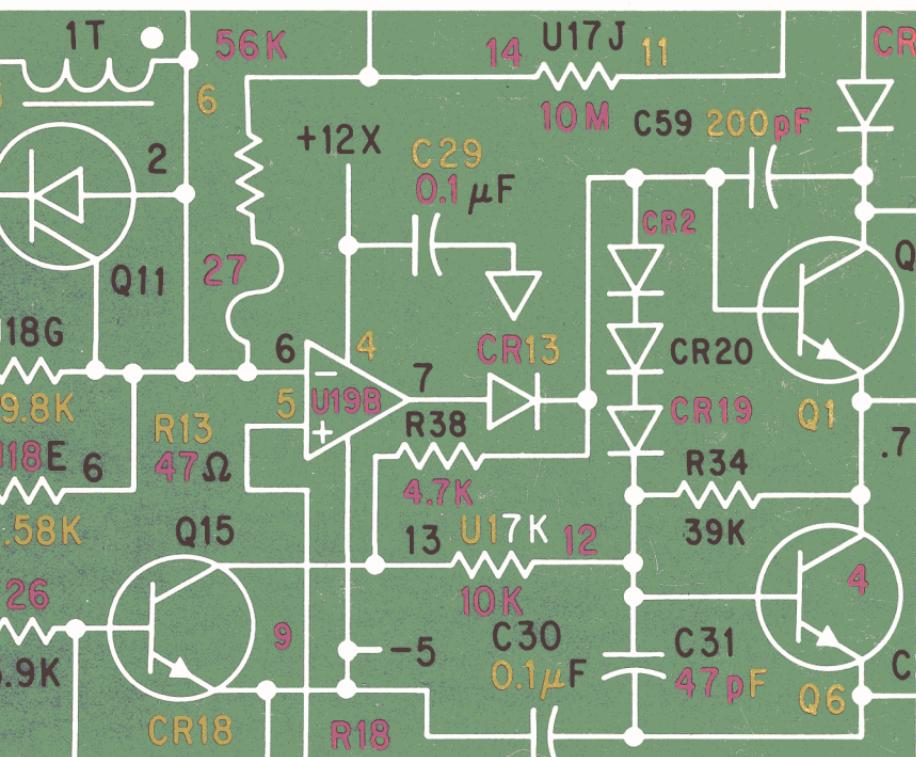


# HEWLETT-PACKARD

Step-by-Step Solutions  
For Your HP Calculator

## Electrical Engineering



HP-42S

 HEWLETT  
PACKARD

# **Electrical Engineering**

---

**Step-by-Step Solutions  
for Your HP-42S Calculator**



Edition 1 November 1988  
Reorder Number 00042-90021

---

## Notice

This book and any keystroke programs contained herein are provided "as is" and are subject to change without notice. **Hewlett-Packard Company makes no warranty of any kind with regard to this book or the keystroke programs contained herein, including, but not limited to, the implied warranties of merchantability and fitness for a particular purpose.** Hewlett-Packard Company shall not be liable for any errors or for incidental or consequential damages in connection with the furnishing, performance, or use of this book or the keystroke programs contained herein.

© Hewlett-Packard Company 1988. All rights reserved. Reproduction, adaptation, or translation of this book, including any programs, is prohibited without prior written permission by Hewlett-Packard Company; except as allowed under the copyright laws. Hewlett-Packard Company grants you the right to use any program contained in this book in a Hewlett-Packard calculator.

The programs that control your calculator are copyrighted and all rights are reserved. Reproduction, adaptation, or translation of those programs without prior written permission of Hewlett-Packard Company is also prohibited.

**Corvallis Division  
1000 N.E. Circle Blvd.  
Corvallis, OR 97330, U.S.A.**

---

## Printing History

**Edition 1**

**November 1988**

**Mfg. No. 00042-90023**

# Contents

---

## 5 How To Use This Book

---

<b>1</b>	<b>7</b>	<b>Circuit Calculations</b>
	<b>8</b>	Voltage Division (“V÷”)
	<b>13</b>	Current Division (“I÷”)
	<b>17</b>	Power Triangle (“PWR3”)
	<b>23</b>	Frequency Response of Transfer Function (“FQRS”)
	<b>28</b>	RC Timing (“RC”)
	<b>32</b>	Delta-Wye Conversions (“DY”)
<hr/>		
<b>2</b>	<b>38</b>	<b>Network Analysis</b>
	<b>39</b>	Using the Circuit Editor (“CIRCT”)
	<b>39</b>	Starting the “CIRCT” Program
	<b>40</b>	Initializing the Circuit
	<b>40</b>	Displaying Circuit Elements
	<b>41</b>	Adding Circuit Elements
	<b>42</b>	Deleting a Circuit Element
	<b>42</b>	Printing the Circuit
	<b>43</b>	Quitting “CIRCT”
	<b>43</b>	Saving Circuits
	<b>43</b>	Storing Elements
	<b>53</b>	Mesh Analysis (“MESH”)
	<b>63</b>	Nodal Analysis (“NODAL”)
	<b>67</b>	Impedance of a Ladder Network (“LADDR”)

---

<b>3</b>	<b>72</b>	<b>Filter Design</b>
	<b>73</b>	Active Filter Design (“AF”)
	<b>82</b>	Butterworth Filter Design (“BF”)
<hr/>		
<b>4</b>	<b>95</b>	<b>Transmission Lines</b>
	<b>96</b>	Transmission Line Calculations (“LINE”)
	<b>108</b>	Transmission Line Impedance (“TLI”)
<hr/>		
<b>5</b>	<b>115</b>	<b>Amplifier Analysis</b>
	<b>116</b>	Transistor Amplifier Performance (“TAP”)
	<b>123</b>	Transistor Amplifier Bias Optimization (“BIAS”)
<hr/>		
<b>6</b>	<b>136</b>	<b>Truth Tables</b>
	<b>137</b>	Writing a Logical Expression as a Program
	<b>139</b>	Printing a Truth Table (“PTTBL”)
	<b>143</b>	An Interactive Truth Table (“ITTBL”)
<hr/>		
<b>7</b>	<b>147</b>	<b>Utilities</b>
	<b>148</b>	Circuit Calculation Utilities
	<b>148</b>	Impedance of an Element (“C→Z” and “L→Z”)
	<b>149</b>	Combining Parallel Impedances (“ZP”)
	<b>149</b>	Entering Radian Frequency (“FQ?”)
	<b>150</b>	Circuit Element Input Utility (“EL?”)
	<b>156</b>	Function Name Utility (“FCN?”)
	<b>157</b>	Yes/No Utility (“Y?N”)
	<b>158</b>	Product Over Sum Utility (“P/S”)
	<b>159</b>	Size Utility (“SIZE?”)

# How To Use This Book

---

Please take a moment to familiarize yourself with the formats used in this book.

**Organization.** Each chapter in this book covers a different area of electrical engineering. Sections within each chapter highlight the use of each program. The sections are organized like this:

- Description of the program, including equations and variables used.
- Special remarks and limitations.
- General instructions.
- Keystroke examples.
- Program listings.

**About the Examples.** Unless otherwise stated, the keystrokes and displays shown in each section assume the following conditions:

- The required programs have been keyed into the calculator.
- The stack is clear and you're using the specified display format. Generally, this does not affect the results of the example, but your displays may not exactly match the ones in this book.
- The SIZE is set to 25 registers (the default). The number of registers needed (if any) is listed under "Remarks."

As you work the examples, remember that lowercase letters are displayed as uppercase letters when they appear in menu labels.

**If You Have a Printer.** Many of the programs in this book will produce printed output if printing is enabled. Press **PRINT** **ON** to enable printing.

If you are not using a printer, be sure to disable printing (**PRINT** **OFF**) to avoid losing results.

**About Program Listings.** It is assumed that you understand how to key programs into your calculator. If you're not sure, review part 2, "Programming," in the owner's manual.

If you print your programs, remember that the printer may print some characters differently than they are displayed. (For example, the  $\downarrow$  character is printed as  $\vee$ .) Also note that some printers cannot print the angle character ( $\angle$ ).

**About the Subject Matter.** Discussions on the various topics included are beyond the scope of this book. Refer to basic texts on the subjects of interest. Many references are available in university libraries and in technical and college bookstores. The examples in this book demonstrate approaches to solving problems, but they do not cover the many ways to approach general problems in electrical engineering.

*Our thanks to Dex Smith of TwentyEighth Street Publishing for developing this book.*


# Circuit Calculations

---

This chapter contains programs that solve for an unknown circuit parameter (when the other parameters are known), define a power triangle from voltage and current, and convert impedances between delta and wye circuit configurations.
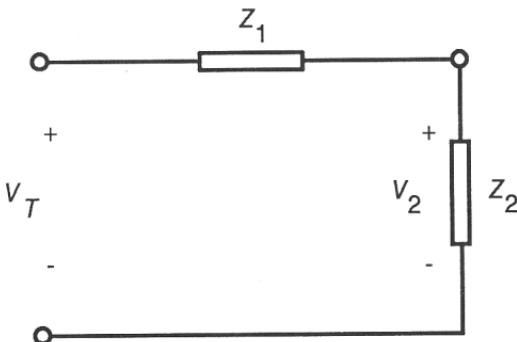
## Voltage Division (“V÷”)

For a circuit in the following general form, the “V÷” program solves for any of the four complex values provided the other three are known.



$$V_2 = \frac{Z_2 V_T}{Z_1 + Z_2}$$

### Variables Used.

In Equation	Description	In Program
$V_T$	Terminal voltage (volts).	VT
$V_2$	Voltage across impedance $Z_2$ .	V2
$Z_1$	Impedance (ohms).	Z1
$Z_2$	Impedance (ohms).	Z2

Since any of these values can be a complex number, the Solver cannot be used. The following program (“V÷”) emulates the Solver by displaying a menu containing the four variables in the above equation.


## Remarks.

- “V÷” does not alter the angular and coordinate modes; you may use them as you wish when keying in complex values.
- Flag 21 (*printer enable*) is set or cleared to match flag 55 (*printer existence*). This automatically produces printer output if flag 55 is set.

## Program Instructions.

1. Key the “V÷” program (listed on page 10) into your calculator.
2. Press **[XEQ] [V÷]** (to run the “V÷” program).
3. Use the variable menu displayed by the program to store the known values.
4. Press the key for the value you want to calculate.
5. To work another problem, go to step 3; to quit, press **[EXIT]**.

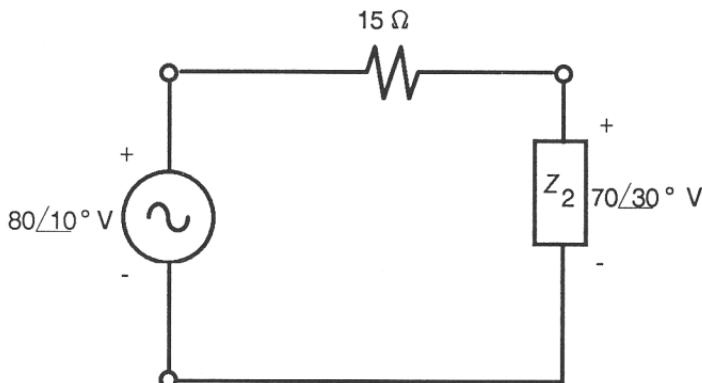**Example.** Given the following circuit and voltage measurements, what must the impedance,  $Z_2$ , be?



Select Degrees and Polar modes, select the FIX 2 display format, and run the “V÷” program.

**[MODES] DEG [MODES] POLAR  
[DISP] FIX 02 [XEQ] [V÷]**

x: 0.00	VT	V2	21	22		
---------	----	----	----	----	--	--

Store the known values.

80 **[ENTER]** 10 **[COMPLEX]** **[VT]**

VT=80.00 $\angle 10.00$	VT	V2	21	22		
-------------------------	----	----	----	----	--	--

15 Z1

Z1=15.00

VT	V2	Z1	Z2

70 [ENTER] 30 [COMPLEX] V2

V2=70.00 <30.00

VT	V2	Z1	Z2

Now, solve for the unknown impedance.

Z2

Z2=37.71 <79.29

VT	V2	Z1	Z2

The unknown impedance ( $Z_2$ ) is  $37.71 \angle 79.29^\circ$  ohms.

### "V÷" Program Listing.

#### Program:

```
00 C 148-Byte Prgm
01 LBL "V÷"
02 MVAR "VT"
03 MVAR "V2"
04 MVAR "Z1"
05 MVAR "Z2"

06 CF 21
07 FS? 55
08 SF 21

09 LBL 00
10 CLA
11 VARMENU "V÷"
12 STOP
```

#### Comments:

Defines menu variables.

Sets or clears flag 21 to match flag 55.

Displays the variable menu and stops.

```
13 RTOX  
14 RTOX  
15 -  
16 XEQ IND ST X  
17 GTO 00
```

Determines which variable was selected by subtracting the ASCII codes of the first two characters in the variable name. For example, when you press **Z1** to calculate  $Z_1$ , the program branches to LBL 41 because the ASCII code of "Z" is 90, the ASCII code of "1" is 49, and  $90 - 49 = 41$ .

```
18 LBL 36  
19 RCL "Z2"  
20 RCL $\times$  "VT"  
21 RCL "Z1"  
22 LASTX  
23 +  
24  $\div$   
25 STO "V2"  
26 VIEW "V2"  
27 RTN
```

Calculates  $V_2$ .

```
28 LBL 02  
29 RCL "Z1"  
30 RCL+ "Z2"  
31 RCL $\times$  "V2"  
32 RCL $\div$  "Z2"  
33 STO "VT"  
34 VIEW "VT"  
35 RTN
```

Calculates  $VT$ .


```
36 LBL 40  
37 RCL "V2"  
38 RCL $\times$  "Z1"  
39 RCL "VT"  
40 LASTX  
41 -  
42  $\div$   
43 STO "Z2"  
44 VIEW "Z2"  
45 RTN
```

Calculates  $Z_2$ .

```
46 LBL 41          Calculates Z1.
47 RCL "Z2"
48 RCL× "VT"
49 RCL÷ "V2"
50 RCL- "Z2"
51 STO "Z1"
52 VIEW "Z1"
53 END
```
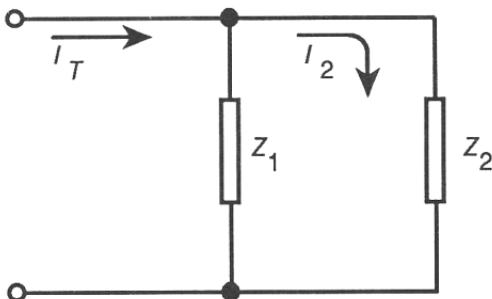
## Current Division (“I÷”)

For a circuit in the following general form, the “I÷” program solves for any of the four complex values provided the other three are known.



$$I_2 = \frac{Z_1 I_T}{Z_1 + Z_2}$$

### Variables Used.

In Equation	Description	In Program
$I_T$	Terminal current (amps).	I.T
$I_2$	Current in impedance $Z_2$ .	I2
$Z_1$	Impedance <sub>1</sub> (ohms).	Z1
$Z_2$	Impedance <sub>2</sub> (ohms).	Z2

Since any of these values can be a complex number, the Solver cannot be used. The following program (“I÷”) emulates the Solver by displaying a menu containing the four variables in the above equation.


## Remarks.

- “I÷” does not alter the angular and coordinate modes. You may use them as you wish when keying in complex values.
- Flag 21 (*printer enable*) is set or cleared to match flag 55 (*printer existence*). This automatically produces printer output if flag 55 is set.

## Program Instructions.

1. Key the “I÷” program (listed on page 15) into your calculator.
2. Press **[XEQ] I÷** (to run the “I÷” program).
3. Use the variable menu displayed by the program to store the known values.
4. Press the key corresponding to the value you want to calculate.
5. To work another problem, go to step 3; to quit, press **[EXIT]**.

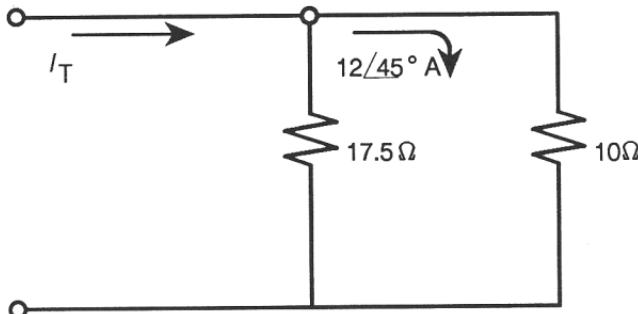**Example.** Given the following circuit, what is the input current ( $I_T$ ) if the current ( $I_2$ ) through the  $10\Omega$  resistor is  $12 \angle 45^\circ$  amperes?



Select Degrees and Polar modes, select the FIX 2 display format, and run the I÷ program.

**[MODES] DEG** **[MODES] POLAR**  
**[DISP] FIX 02** **[XEQ] I÷**

x: 0.00  
I.T I2 21 22

Key in the three known values.

17.5 **Z1**

Z1=17.50  
I.T I2 21 22

10 Z2

Z2=10.00					
I.T	I2	Z1	Z2		

12 [ENTER] 45 [COMPLEX] I2

I2=12.00	∠45.00				
I.T	I2	Z1	Z2		

Now calculate the unknown current.

I.T

I.T=18.86	∠45.00				
I.T	I2	Z1	Z2		

The unknown current ( $I_T$ ) is 18.86 ∠45° amperes.

### “I÷” Program Listing.

#### Program:

```

00 C 155-Byte Prgm
01 LBL "I÷"
02 MVAR "I.T"
03 MVAR "I2"
04 MVAR "Z1"
05 MVAR "Z2"

06 CF 21
07 FS? 55
08 SF 21

09 LBL 00
10 CLA
11 VARMENU "I÷"
12 STOP

13 ATOX
14 ATOX
15 -
16 XEQ IND ST X
17 GTO 00

```

#### Comments:

Defines menu variables.

Sets or clears flag 21 to match flag 55.

Displays the variable menu and stops.

Determines the selected variable by subtracting the ASCII codes of the first two characters in the variable name. For example, when you press **I.T**, the program branches to LBL 27 because the ASCII code of “I” is 73, the ASCII code of “.” is 46, and  $73 - 46 = 27$ .

```

18 LBL 23
19 RCL "Z1"
20 RCLx "I.T"
21 RCL "Z2"
22 LASTX
23 +
24 ÷
25 STO "I2"
26 VIEW "I2"
27 RTN

28 LBL 27
29 RCL "Z2"
30 RCL+ "Z1"
31 RCLx "I2"
32 RCL÷ "Z1"
33 STO "I.T"
34 VIEW "I.T"
35 RTN

36 LBL 40
37 RCL "Z1"
38 RCLx "I.T"
39 RCL÷ "I2"
40 RCL- "Z1"
41 STO "Z2"
42 VIEW "Z2"
43 RTN

44 LBL 41
45 RCL "I2"
46 RCLx "Z2"
47 RCL "I.T"
48 LASTX
49 -
50 ÷
51 STO "Z1"
52 VIEW "Z1"
53 END

```

Calculates *I2*.

Calculates *I.T*.


Calculates *Z2*.

Calculates *Z1*.

## Power Triangle (“PWR3”)


The “PWR3” program calculates any value for the power triangle, provided that certain other values are known.

$$P = VI \cos \theta$$

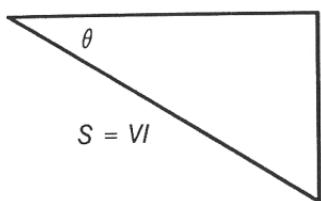

$$Q = VI \sin \theta$$

Lagging

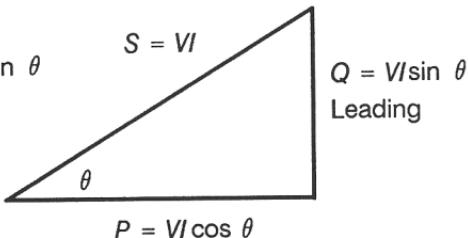

### Variables Used.

In Figure	Description	In Program
$V$	Voltage (volts).	V
$I$	Current (amperes).	I
$P$	Average power (watts).	P
$Q$	Reactive power (vars).	Q
$S$	Apparent power (watts).	S
	Power factor ( $\cos \theta$ ).	Pf

### Remarks.

- Be sure to enter  $V$  and  $I$  as complex numbers. If the values in  $V$  and  $I$  are not complex numbers, the program will stop and display **Invalid Type**. If you generate this error, *restart* the program by pressing **EXIT** **XEQ** **PWR3**.
- The “PWR3” program sets Degrees and Polar modes.

- The “PWR3” program uses flag 10 to control the calculations of  $V$  and  $I$ .
- A minus sign preceding a (result or input) value for power factor indicates a *lagging* power factor.

## Program Instructions.

1. Key the “PWR3” program (listed on page 20) into your calculator.
2. Press **[XEQ] PWR3** (to run the “PWR3” program).
3. Use the variable menu displayed by the program to store the known values and to calculate the unknowns:

To calculate  $P$ ,  $Q$ ,  $S$ , or  $pf$ :

- a. Key in the voltage (in *polar* form) and press **[V]**.
- b. Key in the current (in *polar* form) and press **[I]**.
- c. Calculate any of the four values by pressing **[P]**, **[Q]**, **[S]**, or **[PF]**.

To calculate the voltage,  $V$ :

- a. Key in the current (in *polar* form) and press **[I]**.
- b. Key in the apparent power and press **[S]**.
- c. Key in the power factor and press **[PF]**.
- d. Calculate the voltage by pressing **[V]**.

To calculate the current,  $I$ :

- a. Key in the voltage (in *polar* form) and press **[V]**.
- b. Key in the apparent power and press **[S]**.
- c. Key in the power factor and press **[PF]**.
- d. Calculate the current by pressing **[I]**.

4. To work another problem, go to step 3; to quit, press **[EXIT]**.

**Example.** For a circuit with an applied voltage of  $100 \angle 10^\circ$  volts and a resulting current of  $2.85 \angle -40^\circ$  amperes, determine the power triangle and the power factor.

Select the FIX 2 display format, and run the “PWR3” program.

■DISP ■FIX 02 XEQ PWR3

x: 0.00	V	I	P	Q	S	PF
---------	---	---	---	---	---	----

100 [ENTER] 10 ■COMPLEX ■ V

V=100.00	$\angle 10.00$	V	I	P	Q	S	PF
----------	----------------	---	---	---	---	---	----

2.85 [ENTER] 40 [+/-]  
■COMPLEX ■ I

I=2.85	$\angle -40.00$	V	I	P	Q	S	PF
--------	-----------------	---	---	---	---	---	----

■ P

P=183.19	V	I	P	Q	S	PF
----------	---	---	---	---	---	----

The average power is 183.19 watts.

■ Q

Q=218.32	V	I	P	Q	S	PF
----------	---	---	---	---	---	----

The reactive power is 218.32 vars. (The *sign* of the power factor (PF) indicates if Q is a leading or a lagging value.)

■ S

S=285.00	V	I	P	Q	S	PF
----------	---	---	---	---	---	----

The apparent power is 285 watts.

■ PF

PF=-0.64	V	I	P	Q	S	PF
----------	---	---	---	---	---	----

The power factor is 0.64. Because a minus sign indicates a lagging power factor, the reactive power, Q, is also lagging. If all other variables remain unchanged, what voltage would be required to increase the apparent power to 300 watts?

300 ■ S

S=300.00	V	I	P	Q	S	PF
----------	---	---	---	---	---	----

14

V=105.26 <10.00

The required voltage is  $105.26 \pm 10.00$  volts.

### **“PWR3” Program Listing.**

### Program:

```
00 C 193-Byte Prgm C
01 LBL "PWR3"
02 MVAR "V"
03 MVAR "I"
04 MVAR "P"
05 MVAR "Q"
06 MVAR "S"
07 MVAR "Pf"
08 DEG
09 POLAR
10 CF 21
11 FS? 55
12 SF 21
13 LBL A
14 VARMENU "PWR3"
15 CLA
16 STOP
17 ATOX
18 X=0?
19 GTO A
20 XTOA
21 1
22 AROT
23 R+
24 73
25 -
26 XEQ IND ST X
```

**Comments:**

Declares the menu variables.

Sets Degrees and Polar modes. Sets or clears flag 21 to match flag 55.

Displays variable menu and stops.  
Pressing **R/S** redisplays the menu.

The ASCII character code of the first letter in the variable name is subtracted from 73 to determine which routine to execute.

27	ASTO ST L	Stores the variable name into the Last X-register and displays the result.
28	STO IND ST L	
29	VIEW IND ST L	
30	GTO A	
31	LBL 13	Calculates $V$ .
32	RCL "I"	
33	SF 00	
34	XEQ B	
35	RTN	
36	LBL 00	Calculates $I$ .
37	RCL "V"	
38	CF 00	
39	XEQ B	
40	RTN	
41	LBL 07	Calculates $P$ .
42	XEQ 39	
43	RCL "V"	
44	RCL $\times$ "I"	
45	ABS	
46	RCL $\times$ "Pf"	
47	ABS	
48	RTN	
49	LBL 08	Calculates $Q$ .
50	XEQ 39	
51	XEQ C	
52	RCL "Pf"	
53	ACOS	
54	SIN	
55	$\times$	
56	RTN	
57	LBL 10	Calculates $S$ .
58	XEQ C	
59	ABS	
60	RTN	

```
61 LBL B
62 COMPLEX
63 RCL "pf"
64 FS? 00
65 +/- 
66 ACOS
67 +
68 ENTER
69 ENTER
70 RCL "S"
71 R↑
72 ÷
73 X<>Y
74 COMPLEX
75 FC?C 00
76 +/- 
77 RTN
```

```
78 LBL C
79 RCL "I"
80 RCLX "V"
81 ABS
82 RTN
```

```
83 LBL 39
84 RCL "V"
85 COMPLEX
86 RCL "I"
87 COMPLEX
88 X<>Y
89 R↓
90 -
91 COS
92 LASTX
93 SIGN
94 +/- 
95 ×
96 STO "pf"
97 END
```

Calculates  $V$  if flag 00 is set, or  $I$  if flag 00 is clear.

Calculates the magnitude of  $VT$ .

Calculates  $pf$ .

---

## Frequency Response of Transfer Function (“FQRS”)

For a transfer function of the form

$$G(S) = \frac{K(Z_1S + 1)}{S^N(Z_2S + 1)(Z_3S + 1) \left( \frac{S^2}{\omega_0^2} + \frac{2Z_4S}{\omega_0} + 1 \right)}$$

the “FQRS” program calculates  $G(S)$  and  $\log |G(S)|$  for any input frequency  $\omega$  (where  $S = j\omega$ ).

### Variables Used.

In Equation	Description	In Program
$K$	Transfer function parameter.	K
$N$	Transfer function parameter.	N
$Z_1$	Transfer function parameter.	Z1
$Z_2$	Transfer function parameter.	Z2
$Z_3$	Transfer function parameter.	Z3
$Z_4$	Transfer function parameter.	Z4
$\omega_0$	Transfer function parameter.	ω0
$\omega$	Input frequency, $2\pi f$ (radians/sec).	ω

### Remarks.

- For type 0 systems, enter  $N = 0$ .
- $Z_1, Z_2$ , and  $Z_3$  can be entered as 0. If there is no quadratic term, enter  $Z_4$  as 0 and  $\omega_0$  very large compared to  $1/Z_3$ , where  $Z_3$  is the smallest first-order term used (other than zero).
- The “FQRS” program sets Degrees and Polar modes.

## Program Instructions.

1. Key the “FQRS” program (listed on page 26) into your calculator.
2. Press **[XEQ] FQRS** (to run the “FQRS” program).
3. The program prompts you for values of  $K$ ,  $N$ ,  $Z_1$ ,  $Z_2$ ,  $Z_3$ ,  $Z_4$ , and  $\omega_0$ . At each prompt, key in the value and press **[R/S]**.
4. The program displays  $G(S)$  and  $\log |G(S)|$  and stops. Press **[R/S]** to go to step 3 for another problem.

**Example.** Find  $G(S)$  and  $\log |G(S)|$  for

$$G(S) = \frac{12(S + 0.6)}{S(S + 1)(S^2 + 6S + 36)}$$

The frequency,  $\omega$ , is 0.01 rad/sec.

First put  $G(S)$  into proper form:

$$G(S) = \frac{.2(1.67S + 1)}{S(S + 1) \left[ \left( \frac{S}{6} \right)^2 + \left( \frac{S}{6} \right) + 1 \right]}$$

Select the FIX 2 display format and run the “FQRS” program.

**[DISP] FIX 02 [XEQ] FQRS**

**Y: 0.00  
N?0.00**

**.2 [R/S]**

**Y: 0.20  
N?0.00**

**1 [R/S]**

**Y: 1.00  
Z1?0.00**

**1.67 [R/S]**

**Y: 1.67  
Z2?0.00**

1 [R/S]

Y: 1.00  
Z?0.00

0 [R/S]

Y: 0.00  
Z?0.00

.5 [R/S]

Y: 0.50  
W?0.00

6 [R/S]

Y: 6.00  
W?0.00

.01 [R/S]

G(S)=20.00 4-89.71  
LOG |G(S)|=1.30

$G(S)$  and  $\log |G(S)|$  for the given conditions are 20.00  $\angle -89.71^\circ$  and 1.30.

## **“FQRS” Program Listing.**

### **Program:**

```
00 < 159-Byte Prgm >
01 LBL "FQRS"
02 INPUT "K"
03 INPUT "N"
04 INPUT "Z1"
05 INPUT "Z2"
06 INPUT "Z3"
07 INPUT "Z4"
08 INPUT "w0"

09 LBL 00
10 INPUT "w"
11 DEG
12 RECT
13 1
14 X<>Y
15 RCL÷ "w0"
16 X†2
17 2
18 RCL× "Z4"
19 RCL× "w"
20 RCL÷ "w0"
21 +
22 COMPLEX
23 1
24 RCL "Z3"
25 RCL× "w"
26 COMPLEX
27 ×
28 1
29 RCL "Z2"
30 RCL× "w"
31 COMPLEX
32 ×
33 POLAR
34 COMPLEX
35 90
```

### **Comments:**

Prompts for each input value.


Calculates  $G(S)$ .

```
36 RCLX "N"
37 +
38 +/- 
39 X<>Y
40 RCL "w"
41 RCL "N"
42 Y†X
43 X
44 1/X
45 X<>Y
46 COMPLEX
47 RECT
48 RCL "K"
49 ENTER
50 RCLX "Z1"
51 RCLX "w"
52 COMPLEX
53 X
54 POLAR
55 "G(S)="
56 ARCL ST X
57 ABS
58 LOG
59 ←"LOG |G(S)|="
60 ARCL ST X
61 AVIEW
62 END
                                         Displays results.
```

---
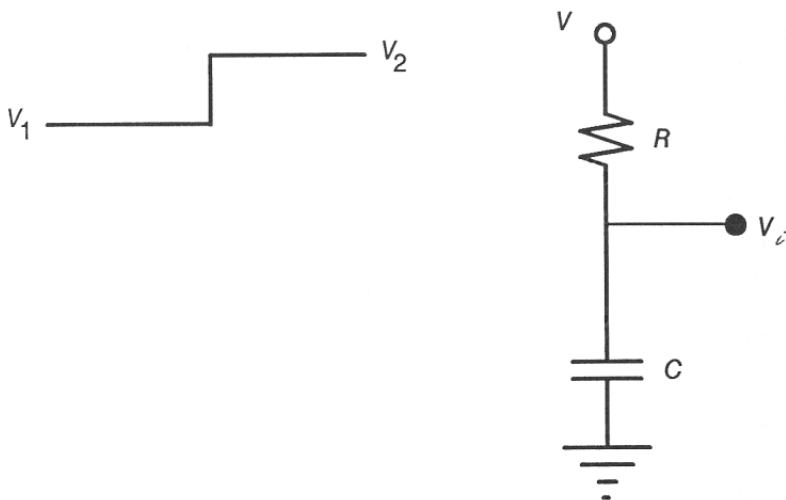
## RC Timing (“RC”)

The “RC” Solver program computes any of the six variables in the following figure and equation, provided the other five are known.



$$V_i = V_1 e^{(-t/RC)} + V_2 \left( 1 - e^{(-t/RC)} \right)$$

By rearranging terms, the equation can be written as:

$$\left( \frac{tC}{\left[ -e \left( 1 - \frac{V_i - V_1}{V_2 - V_1} \right) \right]} \right) - R = 0.$$

where  $e$  is the base of natural logarithms.

## Variables Used.

In Equations	Description	In Program
$V_1$	Voltage before step (volts).	V1
$V_2$	Voltage after step (volts).	V2
$V_i$	Instantaneous voltage (volts).	Vi
$R$	Resistance (ohms).	R
$C$	Capacitance (farads).	C
$t$	Time (seconds).	t

## Remarks.

- The “RC” Solver program uses only *real*-number inputs.
- For voltages across the resistor and capacitor,  $V_R + V_C = V$  applies *at all times*.

## Program Instructions.

1. Key the “RC” Solver program (listed on page 31) into your calculator.
2. Select the “RC” Solver program: press **SOLVER** **RC**.
3. Use the variable menu to store the five known variables: key in the value and press the corresponding key.
4. Press the key corresponding to the unknown variable. The Solver searches for the unknown and displays the solution (if one can be found).
5. To work another problem, go to step 3, or press **EXIT** **EXIT** to quit.

**Example.** A 555 type of integrated circuit timer uses an external RC configuration for time determination. When used as a one-shot, its output pulse terminates when the capacitor charges to two-thirds of the supply voltage. Until the pulse starts, the capacitor is shorted so  $V1 = 0$ . Given a supply voltage of 12V and a  $47\ \mu\text{F}$  capacitor, what size resistor should you use to generate a one-second pulse?

Select the ENG 3 display format and the “RC” Solver program.

■ DISP ENG 03  
■ SOLVER RC

x: 0.000E0  
V1 V2 V1 R C T

0 V1

V1=0.000E0  
V1 V2 V1 R C T

12 V2

V2=12.00E0  
V1 V2 V1 R C T

2 [ENTER] 3 ÷ 12 × V1

V1=8.000E0  
V1 V2 V1 R C T

47 [E] 6 [+/-] C

C=47.00E-6  
V1 V2 V1 R C T

1 T

t=1.000E0  
V1 V2 V1 R C T

R

R=19.37E3  
V1 V2 V1 R C T


Use a 19.37 Kohm resistor.

## **"RC" Program Listing.**

00 < 58-Byte Prgm >	12 RCL "V2"
01 LBL "RC"	13 LASTX
02 MVAR "V1"	14 -
03 MVAR "V2"	15 ÷
04 MVAR "Vi"	16 -
05 MVAR "R"	17 LN
06 MVAR "C"	18 +/-
07 MVAR "t"	19 RCL $\times$ "C"
08 1	20 RCL $\div$ "t"
09 RCL "Vi"	21 1 $\times$
10 RCL "V1"	22 RCL- "R"
11 -	23 END
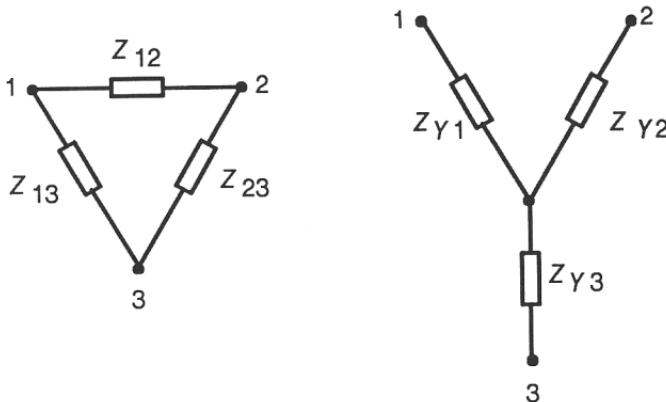
## Delta-Wye Conversions (“DY”)

This program allows you to convert impedance values between delta and wye configurations. That is, given the three wye values ( $Z_{Y1}$ ,  $Z_{Y2}$ , and  $Z_{Y3}$ ), you can calculate any of the three delta values ( $Z_{12}$ ,  $Z_{23}$ , and  $Z_{13}$ ). Likewise, given the delta values, you can calculate any of the wye values.



### Variables Used.

In Figure	Description	In Program
$Z_{Y1}$	Impedance (ohms).	ZY1
$Z_{Y2}$	Impedance (ohms).	ZY2
$Z_{Y3}$	Impedance (ohms).	ZY3
$Z_{12}$	Impedance (ohms).	Z12
$Z_{13}$	Impedance (ohms).	Z13
$Z_{23}$	Impedance (ohms).	Z23

## Remarks.

- Flag 21 (*printer enable*) is set or cleared to match flag 55 (*printer existence*). This automatically produces printer output if flag 55 is set.
- The program will give erroneous results (original inputs) if the *calculated* outputs are used directly as inputs.

## Program Instructions.

1. Key the “DY” program (listed on page 35) into your calculator.
2. Select the coordinate mode you want to use: press **[MODES]** **[RECT]** for Rectangular mode, or **[MODES]** **[POLAR]** for Polar mode.
3. Press **[XEQ]** **[DY]** to run the “DY” program.
4. The program displays a variable menu containing the six variables in the above illustration.

To calculate wye values,


- a. Store each of the three delta values by keying in the value and pressing the corresponding menu key.
- b. Press the key for the wye value you want to calculate. (Repeat for each of the other two unknown wye values.)

To calculate delta values,

- a. Store each of the three wye values by keying in the value and pressing the corresponding menu key.
- b. Press the key for the delta value you want to calculate. (Repeat for each of the other two unknown delta values.)

5. You can work as many problems as you want. The menu stays active until you press **[EXIT]** or select an application menu.

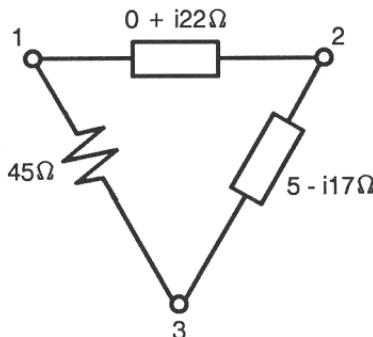**Example.** Given the following delta circuit, determine the equivalent wye circuit.



Select the Rectangular mode and the FIX 4 display format, and run the "DY" program.

**MODES** **RECT** **DISP** **FIX** 04  
**XEQ** **DY**

x: 0.0000  
211 212 213 212 223 213

Enter the delta values.

45 Z13

Z13=45.0000  
211 212 213 212 223 213

0 **ENTER** 22 **COMPLEX** Z12

Z12=0.0000 i22.0000  
211 212 213 212 223 213

5 **ENTER** 17 **+-**  
**COMPLEX** Z23

Z23=5.0000 -i17.0000  
211 212 213 212 223 213

Now calculate each of the wye values.

ZY1

ZY1=1.9604 i19.6040  
211 212 213 212 223 213

ZY2

ZY2=7.6238 i1.4376

ZY1	ZY2	ZY3	Z12	Z23	Z13
-----	-----	-----	-----	-----	-----

ZY3

ZY3=2.9406 -i15.5941

ZY1	ZY2	ZY3	Z12	Z23	Z13
-----	-----	-----	-----	-----	-----

## “DY” Program Listing.

### Program:

```
00 < 219-Byte Prgm >
01 LBL "DY"
02 MVAR "ZY1"
03 MVAR "ZY2"
04 MVAR "ZY3"
05 MVAR "Z12"
06 MVAR "Z23"
07 MVAR "Z13"

08 CF 21
09 FS? 55
10 SF 21

11 LBL A
12 VARMENU "DY"
13 STOP
14 RTOX
15 XTOA
16 RTOX
17 XTOA
18 RTOX
19 XTOA

20 +
21 95
22 -
23 XEQ IND ST X
```

### Comments:

Declares menu variables.

Sets or clears flag 21 to match flag 55.

Returns the ASCII character codes of the selected variable name and restores the name in the Alpha register.

Adds the ASCII codes of the last two characters of the selected variable and subtracts 95 to determine which subroutine to execute.

24 SF 25	Stores the variable name in the Last X register and displays the result.
25 ÷	Division by zero is detected with flag 25 ( <i>error ignore</i> ) and an appropriate message is displayed. If this happens, line 31 is skipped because flag 50 ( <i>message</i> ) is set.
26 RSTO ST L	
27 FC?C 25	
28 XEQ 03	
29 STO IND ST L	
30 FC? 50	
31 VIEW IND ST L	
32 GTO A	
33 LBL 43	Calculates $Z_{Y1}$ .
34 RCL "Z12"	
35 RCLX "Z13"	
36 GTO 01	
37 LBL 44	Calculates $Z_{Y2}$ .
38 RCL "Z12"	
39 GTO 00	
40 LBL 45	Calculates $Z_{Y3}$ .
41 RCL "Z13"	
42 LBL 00	Shared subroutines.
43 RCLX "Z23"	
44 LBL 01	
45 RCL "Z12"	
46 RCL+ "Z13"	
47 RCL+ "Z23"	
48 RTN	
49 LBL 04	Calculates $Z_{12}$ .
50 RCL "ZY3"	
51 GTO 02	
52 LBL 05	Calculates $Z_{13}$ .
53 RCL "ZY2"	
54 GTO 02	
55 LBL 06	Calculates $Z_{23}$ .
56 RCL "ZY1"	

```
57 LBL 02                               Shared subroutine.
58 RCL "ZY1"
59 RCLX "ZY2"
60 LASTX
61 RCLX "ZY3"
62 +
63 RCL "ZY2"
64 RCLX "ZY3"
65 +
66 X<>Y
67 RTN

68 LBL 03                               Division by zero indicates an open
69 F="Open Circuit"                     circuit (infinite resistance). Infinity is
70 9.99E499                         approximated with  $9.99 \times 10^{499}$ .
71 AVIEW
72 END
```

## Network Analysis

---

This chapter contains programs for performing mesh and nodal network analyses for circuits containing any combination of resistors, capacitors, inductors, and general impedances. Circuits for mesh analysis may also contain voltage sources and circuits for nodal analysis may contain current sources.

Circuits are entered into the calculator using the “CIRCT” program and then processed by running the “MESH” or “NODAL” program.

---

## Using the Circuit Editor (“CIRCT”)

“CIRCT” is a menu-driven program that allows you to add, delete, and print elements in a circuit. The circuit elements are stored in a matrix named *CIRCT*, where each row in the matrix contains an element.

**Required Programs.** “CIRCT” (page 45), “EL?” (page 151), and “Y?N” (page 157).

### Starting the “CIRCT” Program

If there are no elements stored in *CIRCT* (if no circuit exists), you’ll see this display when you run the “CIRCT” program:

**[XEQ] CIRCT**

C 0-Element Circuit }			
ADD	DEL	PRINT	INIT

Or, if the matrix *CIRCT* exists, the program assumes that it contains *n* circuit elements (where *n* is the number of rows in the matrix), and you’ll see a display like this:

**[XEQ] CIRCT**

C 7-Element Circuit }			
ADD	DEL	PRINT	INIT

You can view the elements in the circuit by using the **[▲]** and **[▼]** keys.



#### Note

If the *CIRCT* matrix exists but does not contain circuit information that the “CIRCT” program recognizes, the program can be thrown far off course. To prevent this from happening, either clear the *CIRCT* variable (**[CLEAR] CLV CIRCT**) before starting the program, or initialize the circuit as shown in the next section.

---

## Initializing the Circuit

To initialize *CIRCT* (that is, to delete the *CIRCT* matrix), press **INIT** **YES**.

**INIT**

INITIALIZE Circuit?		
YES		NO

**YES**


0-Element Circuit				
ADD				

When there are no circuit elements, note that the **DEL**, **PRINT**, and **INIT** menu keys are *not* displayed or active.

## Displaying Circuit Elements

Use the **▲** and **▼** keys to move up and down through the list of elements.

Here's a typical display:

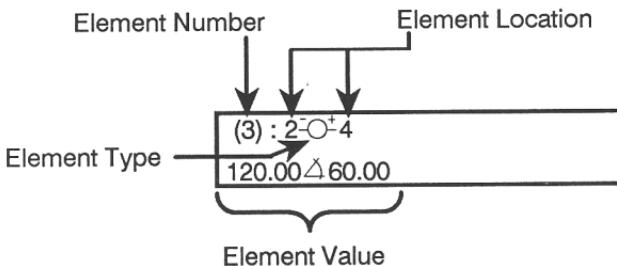

For nodal analysis this display reads: "The third circuit element is a voltage source connected between node 2 and node 4 with a value of 120.00  $\Delta$  60.00° volts." (For mesh analysis, the location numbers would represent *meshes* 2 and 4.)

When a circuit element is displayed, the menu keys **ADD**, **DEL**, **PRINT**, and **INIT** are active even though they are not visible. (If you press **Esc** to clear the message, you'll see that the menu *is* active.)

## Adding Circuit Elements

1. Use the **▲** and **▼** keys to move to the position in the list of circuit elements where you want to add an element. The new element will be inserted *after* the displayed element.
2. Press **HDD**, the *first* menu key. (The menu keys are active, even though the message temporarily covers them.) The program displays **Location: # [ENTER] #** and a menu of the six types of circuit elements.
3. Key in the location of the element.

*For mesh analysis: mesh# [ENTER] mesh#, where the two mesh numbers indicate the meshes that share the element. For an element in a single mesh, press mesh# [ENTER].*

*For nodal analysis: from-node# [ENTER] to-node#, where the circuit element is connected from the first node to the second.*

The order of the location numbers is important only when entering a voltage or current source. For example, the illustration on page 40 shows a voltage *rise* from node 2 to node 4. If the node numbers had been entered in the opposite order, the value should be negative to represent a voltage *drop* from node 4 to node 2.

4. Press a menu key to specify the *type* of element you want to add:

**R** (resistor, ohms)

**C** (capacitor, farads)

**L** (inductor, henrys)

**Z** (general impedance, ohms)

**V** (voltage source, volts)

**I** (current source, amperes)

5. The program displays a menu of the common units for the element you're entering. Key in the value of the element and then press the appropriate key. (For example, to enter a 1,000-ohm resistor you could press 1000 **OHM** or 1 **KOHM**.)

All elements are converted to their default units (see the table on page 44) before being added to *CIRCT*.

To add another element, go to step 3. To return to the main menu, press **EXIT**.

Examples later in this chapter demonstrate how to use the “CIRCT” program for entering circuit elements for mesh and nodal analyses.

## Deleting a Circuit Element

To delete a circuit element:

1. Use the **▲** and **▼** keys to display the element you want to delete.
2. Press **DEL**, the *second* menu key. (The menu keys are active, even though the message temporarily covers them.)
3. To prevent accidentally deleting an element, the program displays **DELETE Element?** Press **YES** to complete the operation. (Press **NO** or **EXIT** if you change your mind.)

## Printing the Circuit

If you want a printed record of the circuit, press **PRINT**, the fifth menu key. Note that this printing is slower than most other printing operations because it involves printing graphics in the display.

The following sample output was printed after entering the circuit on page 54:

( 7-Element Circuit )

```
(1):1 o 1  
150.00 410.00  
(2):1 ~ 1  
16.00  
(3):1 -> 2  
0.00 i20.00  
(4):1 -> 3  
0.00 -i24.00  
(5):2 ~ 2  
32.00  
(6):2 ~ 3  
12.00  
(7):3 -> 3  
0.00 -i16.00
```

## Quitting “CIRCT”

Press **EXIT** to exit the “CIRCT” program. After exiting, if you don’t run any other programs (or move the program pointer in any other way), you can restart “CIRCT” by pressing **R/S**.

## Saving Circuits

To save a copy of your circuit:

1. Press **EXIT** to quit “CIRCT”.
2. Press **RCL** **CIRCT** to recall a copy of *CIRCT*.
3. Press **STO** **ENTER** *name* **ENTER** to store a copy of *CIRCT* (where *name* is the name of a new variable).
4. Press **R/S** to restart the “CIRCT” program.

To restore a saved copy of a circuit:

1. Press **EXIT** to quit “CIRCT”.
2. Press **RCL** ***name*** to recall a copy of a circuit that’s been saved.
3. Press **STO** **CIRCT** to store a copy of the matrix into *CIRCT*.
4. Press **R/S** to restart the “CIRCT” program.

## Storing Elements

The *CIRCT* variable contains a three-column matrix. Each row in the matrix represents a single circuit element:

- The first column contains a number in the form *tt.mnnn* where *tt* is the type code for the element (see the table below), *mm* is the first location number, and *nn* is the second location number. If *tt.mnnn* is negative, the value for the element is complex.
- The second column contains the *real* value of the element in the default units (see the table below). Voltage and current sources are stored in Polar form; all other elements are stored in Rectangular form.
- The third column contains the *imaginary* part of the element value.

Element Type	Units	Type Code
Resistor	Ohms	82
Capacitor	Farads	67
Inductor	Henrys	76
General impedance	Ohms	90*
Voltage source	Volts	86*
Current source	Amperes	73*

\*If the element value is a complex number, the type code is negative.

## Remarks.

- *CIRCT* is an  $n \times 3$  matrix containing the circuit elements. An example of entering the elements of a circuit is contained in the next section, “Mesh Analysis.”
- Values for all elements are displayed using the default units (see the table above).
- Flag 09 is set when the editor is extracting a complex value from *CIRCT*.
- Flag 10 is set if there is no variable *CIRCT*.
- Flag 25 is used to determine if *CIRCT* exists.
- Register  $R_{00}$  contains the current circuit-element number.
- Register  $R_{01}$  contains the total number of circuit elements.

## “CIRCT” Program Listing.

### Program:

```
00 C 626-Byte Prgm >
01 LBL "CIRCT"
02 PROFF
03 CLX
04 STO 00
05 STO 01
06 CF 10
07 SF 25
08 INDEX "CIRCT"
09 FC?C 25
10 SF 10
11 FS? 10
12 GTO A
13 RCL "CIRCT"
14 DIM?
15 X<>Y
16 STO 01

17 LBL A
18 CLMENU
19 "ADD"
20 KEY 1 GTO 01
21 "DEL"
22 FC? 10
23 KEY 2 GTO 02
24 "PRINT"
25 FC? 10
26 KEY 5 XEQ 12
27 "INIT"
28 FC? 10
29 KEY 6 GTO 06
30 KEY 7 XEQ 07
31 KEY 8 XEQ 08
32 KEY 9 GTO 99
```

### Comments:

Initializes the program.

Defines the menu for the program. If flag 10 is set (no circuit), defines only the “ADD” key.

33 LBL B	Displays the menu and stops.
34 XEQ 00	
35 MENU	
36 STOP	
37 GTO B	
38 LBL 01	
39 XEQ "EL?"	Inputs a circuit element using the "EL?" utility on page 151.
40 FC?C 08	
41 GTO A	
42 FS? 10	
43 1	Inserts the new circuit element into the <i>CIRCT</i> matrix.
44 FS?C 10	
45 GTO 03	
46 RCL 00	
47 X=0?	
48 GTO 10	
49 RCL 01	
50 X=Y?	
51 GTO 05	
52 R+	
53 R+	
54 RCL "CIRCT"	
55 DIM?	
56 R+	
57 1	
58 +	
59 LBL 03	
60 3	Increases (or creates) the <i>CIRCT</i> matrix for the new element.
61 DIM "CIRCT"	
62 INDEX "CIRCT"	
63 LBL 04	
64 CLX	Stores the new circuit element into <i>CIRCT</i> .
65 1	
66 STOIJ	
67 R+	
68 R+	

```
69 X<>Y
70 +
71 X<>Y
72 REAL?
73 GTO 11
74 COMPLEX
75 X<>Y
76 +
77 X<>Y
78 LBL 11
79 STOEL
80 RCLIJ
81 X<>Y
82 STO 00
83 1
84 STO+ 01
85 GTO 01
```

```
86 LBL 05
87 I+
88 INSR
89 R+
90 R+
91 RCLIJ
92 GTO 04
```

```
93 LBL 10
94 R+
95 1
96 ENTER
97 STOIJ
98 INSR
99 GTO 04
```

Inserts a new row into the *CIRCT* matrix.

Inserts a new row at the top of the *CIRCT* matrix.

100 LBL 00	
101 RCL 00	
102 IP	
103 X=0?	
104 GTO C	
105 FS? 10	
106 GTO C	
107 "<"	
108 AIP	
109 ←":"	
110 1	
111 STOIJ	
112 RCLEL	
113 CF 09	
114 X<0?	
115 SF 09	
116 ABS	
117 IP	
118 LASTX	
119 FP	
120 100	
121 X	
122 IP	
123 AIP	
124 LASTX	
125 FP	
126 100	
127 X	
128 ← " "	
129 AIP	
130 ← "t"	
131 J+	
132 R+	
133 R+	
134 RECT	
135 86	
136 X=Y?	
137 POLAR	
138 R+	

139 73  
140 X=Y?  
141 POLAR  
142 R $\downarrow$   
143 RCLEL  
144 ENTER  
145 FS? 09  
146  $\Rightarrow$   
147 FS?C 09  
148 COMPLEX  
149 ARCL ST X  
150 AVIEW  
151 REAL?  
152 R $\downarrow$   
153 R $\downarrow$   
154 1  
155 ENTER  
156 32  
157 POSA  
158 6  
159 X  
160 4  
161 +  
162 XEQ IND ST T  
163 AGRAPH  
164 RTN  
  
165 LBL C  
166 RCL 01  
167 " $\langle$  "  
168 RIP  
169  $\vdash$ "-Element "  
170  $\vdash$ "Circuit ?"  
171 AVIEW  
172 RTN  
  
173 LBL 82  
174 " $\leftrightarrow$  $\wedge$  $\wedge$   $\wedge$  $\wedge$  $\wedge$ "  
175 RTN

Displays top-of-list message.

Alpha string to produce graphic resistor.

176 LBL 67  
177 "++++|÷|++++"  
178 RTN

179 LBL 76  
180 "↔↔"  
181 4  
182 XTOA  
183 ←"E"  
184 XTOA  
185 ←"E↔↔"  
186 R↓  
187 RTN

188 LBL 90  
189 "↔↔8((((8↔↔"  
190 RTN

191 LBL 86  
192 "fff£8DDD8£££"  
193 RTN

194 LBL 73  
195 "↔↔8DDD8£T8↔"  
196 RTN

197 LBL 02  
198 RCL 00  
199 X=0?  
200 GTO A  
201 "DELETE Element?"  
202 XEQ "Y?N"  
203 X=0?  
204 GTO A  
205 SF 25  
206 DELR  
207 FC?C 25  
208 GTO 14  
209 RCLIJ  
210 X<>Y

Alpha string to produce graphic capacitor.

Alpha strings to produce graphic inductor.

Alpha string to produce graphic impedance.

Alpha string to produce graphic voltage source.

Alpha string to produce graphic current source.

Deletes the current circuit element.

```
211 STO 00
212 1
213 STO- 01
214 GTO A

215 LBL 06
216 "INITIALIZE "
217 ←"Circuit?""
218 XEQ "Y?N"
219 X=0?
220 GTO A
221 LBL 14
222 CLV "CIRCT"
223 CLX
224 STO 00
225 STO 01
226 SF 10
227 GTO A

228 LBL 07
229 RCL 00
230 1
231 -
232 X<0?
233 RCL 01
234 STO 00
235 RTN

236 LBL 08
237 1
238 STO+ 00
239 RCL 01
240 RCL 00
241 X>Y?
242 CLX
243 STO 00
244 RTN
```

Initializes the pointers and deletes *CIRCT* variable.

Decrements the element pointer.

Increments the element pointer.

245	LBL	12	Prints the graphic display for circuit elements in <i>CIRCT</i> .
246	RCL	01	
247	1E-3		
248	X		
249	STO	00	
250	LBL	13	
251	XEQ	00	
252	PRON		
253	PRLCD		
254	CLA		
255	PRA		
256	PROFF		
257	ISG	00	
258	GTO	13	
259	CLX		
260	STO	00	
261	RTN		
262	LBL	99	Exits all menus.
263	EXITALL		
264	END		

## Mesh Analysis (“MESH”)

The “MESH” program (listed on page 57) calculates the mesh currents of a circuit containing any combination of resistors, capacitors, inductors, general impedances, and voltage sources. (If the circuit you want to analyze contains *current* sources, convert them to voltage sources.)

**How “MESH” Works.** “MESH” uses the elements in the *CIRCT* matrix to create the following matrices:

$$\mathbf{I} = \frac{\mathbf{Z}}{\mathbf{V}} = \frac{\mathbf{MATA}}{\mathbf{MATB}} = \mathbf{MATX}$$

### Variables Used.

In Equation	Description	In Program
	$n \times 3$ matrix containing circuit elements.	CIRCT
<b>Z</b>	Impedance matrix, <b>Z</b> .	MATA
<b>V</b>	Voltage matrix, <b>V</b> .	MATB
<b>I</b>	Solutions matrix.	MATX
	Radian frequency, $2\pi f$ (radians/sec).	w

Since the variable names *MATA*, *MATB*, and *MATX* are used, you can use the Simultaneous Equations application to work with the data after using “MESH”. Press **MATRIX** **SIMQ nn** (where *nn* is the number of mesh currents).

### Remarks.

- Flag 08 is cleared for mesh analysis.
- Flag 10 is set when the location numbers are equal (for mesh analysis).
- “MESH” leaves the calculator in the Polar mode.
- Register  $R_{00}$  contains the element counter. Register  $R_{02}$  contains the number of mesh currents. Register  $R_{03}$  is used for intermediate


results. Be sure to set the SIZE to at least four registers ( **MODES** **SIZE** 4 **ENTER** ) before running “MESH”.

**Programs Required.** “MESH” (page 57), “CIRCT” (page 45), “C→Z” (page 148), “EL?” (page 151), “FQ?” (page 149), and “Y?N” (page 157).

### Program Instructions.

1. Enter the circuit elements using the “CIRCT” program. Press **EXIT** when you are finished.
2. If you want the results to be printed, press **PRINT** **POFF** to enable printing. If you’re *not* using a printer, be sure to disable printing (press **PRINT** **POFF**).
3. Press **XEQ** **MESH** (to run the “MESH” program).
4. When you see **No. Mesh Currents?**, key in the number of mesh currents and press **R/S**.
5. When you see **Radian Frequency( $2\pi f$ )?**, key in the radian frequency and press **R/S**. (This value is used only if the circuit contains capacitance or inductance.)
6. The mesh currents are then calculated and displayed. If you’re not using a printer, press **R/S** after each result is displayed.

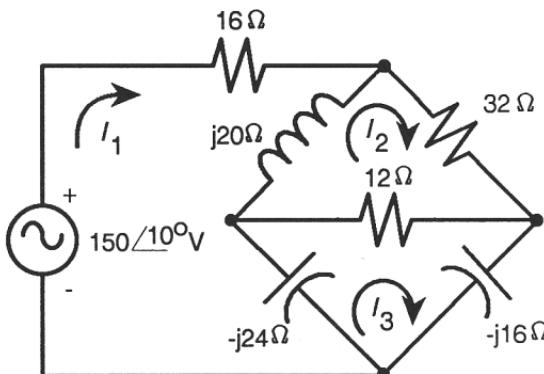**Example: Calculating Mesh Currents.** Use the “CIRCT” program to enter the following circuit. Then execute “MESH” to calculate the mesh currents,  $I_1$ ,  $I_2$ , and  $I_3$ .



First, select FIX 2 display format and then enter the circuit elements using the “CIRCT” program.

■ [DISP] FIX 02 [XEQ] CIRCT

{ 7-Element Circuit }  
ADD DEL PRINT INIT

If the circuit contains any elements, delete them by initializing it.

INIT YES

{ 0-Element Circuit }  
ADD

Now, add the new elements to the circuit.

ADD

Location: # [ENTER] #  
R C L Z V I

Enter all of the elements in mesh 1. Since the voltage source isn't shared by another mesh, its location is entered like this:

1 [ENTER] V

Value?  
MV V KV

Enter the value for the voltage source.

150 [ENTER] 10 ■ [COMPLEX] V

Location: # [ENTER] #  
R C L Z V I

Enter the location and value for the 16-ohm resistor. Like the voltage source, the resistor is unique to mesh 1, so its location is entered the same way (1 [ENTER]).

1 [ENTER] R 16 OHM

Location: # [ENTER] #  
R C L Z V I

Since a complex impedance is provided for the inductor, enter it as a general impedance. This element is shared between mesh 1 and mesh 2, so enter both location numbers.

1 [ENTER] 2 Z 0 [ENTER] 20  
■ [COMPLEX] OHM

Location: # [ENTER] #  
R C L Z V I

Enter the capacitor shared by mesh 1 and mesh 3 in the same way.

1 [ENTER] 3 Z 0 [ENTER] 24  
+/- ■ [COMPLEX] OHM

Location: # [ENTER] #  
R C L Z V I

Now enter the elements in mesh 2 that have not already been entered.

2 [ENTER] R 32 OHM

Location: #		[ENTER]	#		
R	C	L	2	V	I

2 [ENTER] 3 R 12 OHM

Location: #		[ENTER]	#		
R	C	L	2	V	I

Enter the last element, which is the capacitor unique to mesh 3. (Note that you could have entered these elements in any order.)

3 [ENTER] Z 0 [ENTER] 16  
+/- [COMPLEX] OHM

Location: #		[ENTER]	#		
R	C	L	2	V	I

Press [EXIT] to return to the main level. You'll see the last element that you entered.

[EXIT]

(?)	:3	3	0.00	-i16.00
-----	----	---	------	---------

At this point you can use **▲** and **▼** to view the elements in the circuit.

Exit from the "CIRCT" program and calculate the mesh currents. If you want the results printed, press [PRINT] **▲** **POH** to enable printing.

[EXIT]

y: 1.00
x: 34.00

[XEQ] MESH

No. Mesh Currents?
x: 0.00

Key in the number of mesh currents.

3 [R/S]

Radian Frequency( $2\pi f$ )?
x: 0.01

Since the inductor and capacitors were given as complex impedances, the frequency will *not* be used. Press [R/S] to display the current in mesh 1.

[R/S]

I1=
x: 6.28 <4.72

If you're not using a printer, press **R/S** to display the current in mesh 2.

**R/S**

I2=  
x: 2.61 <53.37

If you're not using a printer, press **R/S** again to display the current in mesh 3.

**R/S**

I3=  
x: 3.09 <-2.73

## **"MESH" and "NODAL" Program Listing.**

### **Program:**

```
00 C 491-Byte Prgm
01 LBL "MESH"
02 CF 08
03 "No. Mesh "
04 P"Currents?"
05 GTO A

06 LBL "NODAL"
07 SF 08
08 "No. Nodes?"

09 LBL A
10 RCL 02
11 PROMPT
12 STO 02

13 ENTER
14 NEWMAT
15 ENTER
16 COMPLEX
17 STO "MATA"
18 DIM?
19 1
20 STO 00
21 NEWMAT
22 ENTER
23 COMPLEX
24 STO "MATB"
25 XEQ "FQ?"
```

### **Comments:**

Clears flag 08 (to indicate mesh analysis) and prompts for the number of mesh currents.

Sets flag 08 (to indicate nodal analysis) and prompts for the number of nodes.

Stores the number of mesh currents or nodes.

Creates the complex matrices *MATA* and *MATB*, and prompts for a frequency.

```
26 CF 21
27 "Working...."
28 AVIEW
29 FS? 55
30 SF 21

31 LBL a
32 INDEX "CIRCT"
33 RCL 00
34 1
35 SF 25
36 STOIJ
37 FC?C 25
38 GTO D

39 RCLEL
40 XEQ IND ST X

41 1
42 STO+ 00
43 GTO a

44 LBL B
45 FS? 08
46 1/X
47 ENTER
48 R+
49 R+
50 INDEX "MATA"
51 STOIJ
52 RCLEL
53 R+
54 FS? 10
55 GTO b
56 -
57 STOEL
58 R+
59 X<>Y
60 STOIJ
61 R+
```

Displays a "working" message and sets or clears flag 21 to match flag 55.

Sets the index pointer to the current element (identified in  $R_{00}$ ). If this generates an error, then the end of the *CIRCT* matrix has been reached.

Recalls the element type code and executes the appropriate subroutine to add the element value to *MATA* and *MATB*.

Increments the element pointer and repeats the loop for the next element.

Accumulates an element value into *MATA*. If flag 10 is set (indicating an element shared by two meshes or connected to the reference node), adds the value only to the matrix element on the main diagonal. If flag 10 is clear, the value is accumulated to the appropriate matrix elements not on the diagonal. Note that values accumulated along the diagonal are positive; values accumulated in other matrix elements of *MATA* are negative.

62	STOEL	
63	CLX	
64	LASTX	
65	R↑	
66	STO 03	
67	R↑	
68	ENTER	
69	STOIJ	
70	R↓	
71	RCLEL	
72	R↑	
73	XEQ b	
74	RCL 03	
75	ENTER	
76	STOIJ	
77	RCLEL	
78	LASTX	
79	LBL b	Stores a value into the matrix.
80	+	
81	STOEL	
82	RTN	
83	LBL 82	Stores a resistor value.
84	XEQ F	
85	XEQ e	
86	GTO B	
87	LBL 67	Stores a capacitor value.
88	XEQ F	
89	XEQ e	
90	XEQ "C→Z"	
91	GTO B	
92	LBL 76	Stores an inductor value.
93	XEQ F	
94	XEQ e	
95	XEQ "L→Z"	
96	GTO B	
97	LBL 90	Stores a general impedance value.
98	XEQ F	

99 XEQ e  
100 XEQ e  
101 RECT  
102 COMPLEX  
103 GTO B

104 LBL 73  
105 LBL 86  
106 XEQ F  
107 XEQ e  
108 XEQ e  
109 POLAR  
110 COMPLEX  
111 INDEX "MATB"  
112 RCL ST Z  
113 FC? 08  
114 GTO c  
115 FC? 10  
116 GTO c  
117 X#0?  
118 GTO C  
119 X<> ST Z  
120 X<>Y  
121 -1  
122 x  
123 X<>Y

124 LBL C  
125 1  
126 STOIJ  
127 RCLEL  
128 R↑  
129 +  
130 STOEL  
131 RTN

132 LBL c  
133 1  
134 STOIJ  
135 CLX  
136 RCL ST T

Stores a current or voltage source into *MATB*. Since the two types are not distinguished, all sources are assumed to be voltage sources for mesh analysis or current sources for nodal analysis.

Adds a current source connected to the reference node.

Adds a voltage source (mesh analysis) or a current source *not* connected to the reference node (nodal analysis).

```
137 ENTER
138 RCLEL
139 R+
140 +
141 STOEL
142 R+
143 X=Y?
144 RTN
145 1
146 STOIJ
147 RCLEL
148 LASTX
149 -
150 STOEL
151 RTN

152LBL D
153 POLAR
154 RCL "MATB"
155 RCL÷ "MATA"
156 STO "MATX"

157 SF 21
158 INDEX "MATX"

159LBL d
160 RCLIJ
161 R+
162 "I"
163 FS? 08
164 "V"
165 AIP
166 ←"="
167 RCLEL
168 FS? 55
169 ARCL ST X
170 AVIEW

171 I+
172 FC? 77
173 GTO d
174 RTN
```

Calculates the results using matrix division.

Prepares to display the results.

Recalls each result from *MATX* and displays it with the appropriate label. If a printer is being used (flag 55 set), the value is appended to the label.

Flag 77 is tested to determine when the end of *MATX* has been reached.

175 LBL e	Increments the column pointer and recalls a matrix element.
176 J+	
177 RCLEL	
178 RTN	
179 LBL F	Decodes the element location into two mesh or node numbers in the X- and Y-registers.
180 ABS	
181 FP	
182 100	
183 x	
184 IP	
185 LASTX	
186 FP	
187 100	
188 x	
189 CF 10	Sets flag 10 to indicate that the two location numbers are the same.
190 X=Y?	
191 SF 10	
192 FC? 08	
193 RTN	
194 FS? 10	For nodal analysis (flag 08 set), displays an error message if the location numbers are equal. (The numbers do not make sense if they're equal.)
195 GTO J	
196 XEQ G	
197 XEQ G	
198 X<>Y	
199 FC? 10	
200 RTN	
201 +	
202 ENTER	
203 RTN	
204 LBL G	Sets flag 10 if the reference node is used.
205 X=0?	
206 SF 10	
207 X<>Y	
208 RTN	
209 LBL J	Error message.
210 "Invalid Data"	
211 PROMPT	
212 END	

## Nodal Analysis (“NODAL”)

The “NODAL” program (listed on page 57) calculates the node voltages of a circuit containing any combination of resistors, capacitors, inductors, general impedances, and current sources. (If the circuit you want to analyze contains *voltage* sources, convert them to current sources.)

**How “NODAL” Works.** “NODAL” uses the circuit information in the *CIRCT* matrix to create the following matrices:

$$\mathbf{V} = \frac{\mathbf{Z}}{\mathbf{I}} = \frac{\mathbf{MATA}}{\mathbf{MATB}} = \mathbf{MATX}$$

### Variables Used.

In Equation	Description	In Program
<b>Z</b>	$n \times 3$ matrix containing circuit elements.	<i>CIRCT</i>
<b>V</b>	Impedance matrix.	<i>MATA</i>
<b>I</b>	Voltage matrix.	<i>MATX</i>
	Current matrix.	<i>MATB</i>
	Radian frequency, $2\pi f$ (radians/sec).	<i>w</i>

Since the variable names *MATA*, *MATB*, and *MATX* are used, you can use the Simultaneous Equations application to work with the data after you've finished using “NODAL”. Press **MATRIX** **SIMQ** *nn* (where *nn* is the number of nodes).

### Remarks.

- Flag 08 is set for nodal analysis.
- Flag 10 is set when one location number is zero (for nodal analysis).
- “NODAL” leaves the calculator in Polar mode.
- Register  $R_{00}$  contains the element counter. Register  $R_{02}$  contains the number of nodes. Register  $R_{03}$  is used for intermediate results. Be


sure to set the SIZE to at least four registers (■ **MODES** ▼ **SIZE** 4 **ENTER**) before running “NODAL”.

**Programs Required.** “MESH” (page 57), “CIRCT” (page 45), “C→Z” (page 148), “EL?” (page 151), “FQ?” (page 149), “Y?N” (page 157).

### Program Instructions.

1. Enter the circuit elements using the “CIRCT” program. Press **EXIT** when you’re finished.
2. If you want the results to be printed, press ■ **PRINT** ▲ **PON** to enable printing. If you’re *not* using a printer, be sure to press ■ **PRINT** ▲ **POFF** to disable printing.
3. Press **XEQ** **NODAL** (to run the “NODAL” program).
4. When you see **No. Nodes?**, key in the number of nodes and press **R/S**.
5. When you see **Radian Frequency( $2\pi f$ )?**, key in the radian frequency and press **R/S**. (This value is used only if the circuit contains capacitance or inductance.)
6. The node voltages are then calculated and displayed. If you’re not using a printer, press **R/S** after each result is displayed.

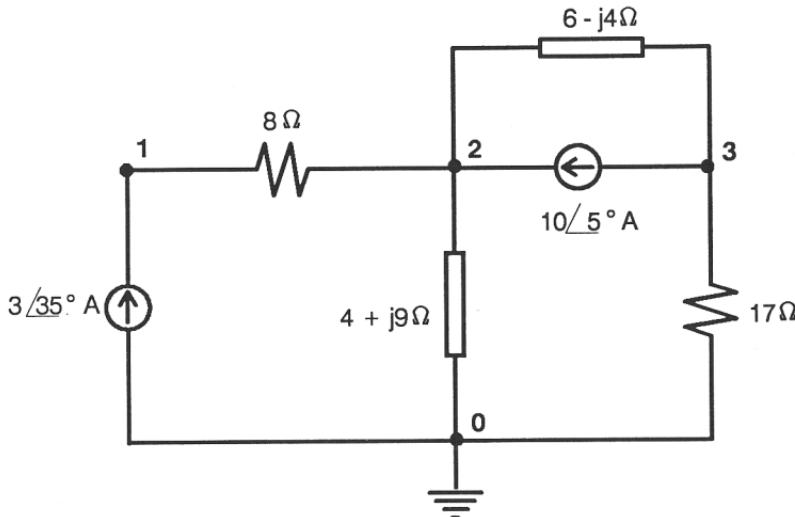**Example: Calculating Node Voltages.** Use the “CIRCT” program to enter the following circuit. Then execute “NODAL” to calculate the node voltages,  $V_1$ ,  $V_2$ , and  $V_3$ .



Begin by selecting FIX 2 display format and running “CIRCT”.

■DISP FIX 02 XEQ CIRCT

{ 7-Element Circuit }

ADD DEL

PRINT INIT

If “CIRCT” has any elements stored in it, delete them by initializing it.

INIT YES

{ 0-Element Circuit }

ADD

Now, add the new elements to the circuit.

ADD

Location: # [ENTER] #

R C L Z V I

Enter the current source from node 0 to node 1.

0 [ENTER] 1 I 3 [ENTER] 35

Location: # [ENTER] #

■COMPLEX A

R C L Z V I

Enter the resistor from node 1 to node 2.

1 [ENTER] 2 R 8 OHM

Location: # [ENTER] #

R C L Z V I

Enter the impedance from node 0 to node 2.

0 [ENTER] 2 Z 4 [ENTER] 9

Location: # [ENTER] #

■COMPLEX OHM

R C L Z V I

Enter the resistor from node 0 to node 3.

0 [ENTER] 3 R 17 OHM

Location: # [ENTER] #

R C L Z V I

Enter the current source from node 3 to node 2. (Note that if you entered this source from node 2 to node 3, the *sign* is reversed:  $-10 \Delta 5^\circ A$ .)

3 [ENTER] 2 I 10 [ENTER]

Location: # [ENTER] #

5 ■COMPLEX A

R C L Z V I

Enter the impedance from node 2 to node 3.

2 [ENTER] 3 Z 6 [ENTER]

Location: # [ENTER] #

4 [+/-] ■COMPLEX OHM

R C L Z V I

Press **EXIT** to return to the program's main menu.

**EXIT**

(6):2  $\leftarrow$  3  
6.00 -i4.00

At this point you can use **▲** and **▼** to view the elements in the circuit. Exit the "CIRCT" program and calculate the node voltages. If you want the results printed, press **PRINT** **▲** **►** **PON** to enable printing.

**EXIT**

y: 1.00  
x: 34.00

**XEQ** **NODA**

No. Nodes?  
x: 0.00

Key in the number of nodes. (Do not include the reference node).

3 **R/S**

Radian Frequency( $2\pi f$ )?  
x: 0.01

Since no capacitors or inductors were entered, the frequency is not needed; press **R/S** to calculate the results.

**R/S**

V1=  
x: 68.66  $\angle$ 47.03

If you're not using a printer, press **R/S** to display the voltage at node 2.

**R/S**

V2=  
x: 45.46  $\angle$ 53.34

If you're not using a printer, press **R/S** again to display the voltage at node 3.

**R/S**

V3=  
x: 58.07  $\angle$ 126.80

---

## Impedance of a Ladder Network (“LADDR”)

This program calculates the input impedance,  $Z_{in}$ , of a ladder network. Elements are added one at a time starting with the element furthest from the terminals where  $Z_{in}$  is measured. The first element must be connected in parallel.

Given an input *admittance* of  $Y_{in}$ , adding a shunt (parallel)  $R$ ,  $L$ , or  $C$  results in a new input impedance:

$$Y_{new} = \begin{cases} Y_{in} + \left( \frac{1}{R_p} + j0 \right) \\ Y_{in} + \left( 0 - j \frac{1}{\omega L_p} \right) \\ Y_{in} + (0 + j\omega C_p) \end{cases}$$

Adding a series  $R$ ,  $L$ , or  $C$ , we have:

$$Y_{new} = \begin{cases} \left( \frac{1}{Y_{in}} + (R_s + j0) \right)^{-1} \\ \left( \frac{1}{Y_{in}} + (0 + j\omega L_s) \right)^{-1} \\ \left( \frac{1}{Y_{in}} + \left( 0 - j \frac{1}{\omega C_s} \right) \right)^{-1} \end{cases}$$

where  $Y = 1/Z$  and  $\omega = 2\pi f$ .

**Variable Used.**  $Z_{in}$  is the impedance looking into the ladder network.

### Remarks.

- Elements are entered in rectangular form; however, the input impedance is displayed in polar form. (If you want the impedance displayed in rectangular mode, you can change line 29 of the “LADDR” program listing to 29 RECT and then delete line 31.)

- If a circuit element is given as a complex impedance, key in the complex value and then add it to the circuit using **RF** and **RS**.
- Flag 00 is set when  $Z_{in} = 0$ .
- Flag 21 (*printer enable*) is set or cleared to match flag 55 (*printer existence*). This automatically produces printer output if flag 55 is set.

**Programs Required.** “LADDR” (page 70), “C→Z” (page 148), and “FQ?” (page 149).

### Program Instructions.

1. Key the required programs into your calculator.
2. Press **XEQ LADDR** (to run the “LADDR” program).
3. When you see **Radian Frequency(2πf)?**, key in the radian frequency and press **R/S**. (If the correct frequency is already in the X-register, just press **R/S**.)
4. The program displays a menu of the elements that can be added. For each element in the network (starting with the element furthest from the terminals where  $Z_{in}$  is measured), key in the value of the element and then press the corresponding key.

**RF** (parallel resistor, ohms)

**LF** (parallel inductor, henrys)

**CP** (parallel capacitor, farads)

**RS** (series resistor, ohms)


**LS** (series inductor, henrys)

**CS** (series capacitor, farads)

The series elements are not displayed until the first parallel element has been entered. Each time you add an element, the new impedance is displayed.

5. To quit, press **EXIT**. After quitting, you can restart “LADDR” by pressing **R/S**.

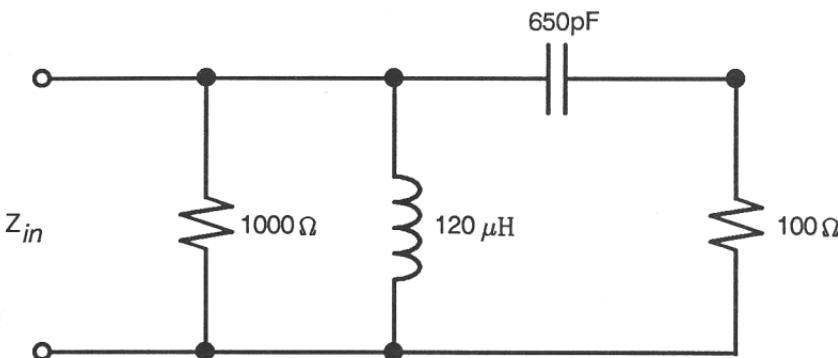**Example.** Find the input impedance of the following circuit at a frequency of 1 MHz:



Select the FIX 2 display format and run the “LADDR” program.

■DISP FIX 02 XEQ LADDR

Radian Frequency( $2\pi f$ )?  
x: 0.01

The frequency is given in Hz. Convert it to radians/second.

E 6 ■π x 2 x R/S

Zin=0.00 40.00  
RP LP CP RS LS CS

Enter the four elements (working *right to left*). Notice that the current value of  $Z_{in}$  is displayed after each element is entered.

100 ■ RP

Zin=100.00 40.00  
RP LP CP RS LS CS

650 E 12 +/- CS

Zin=264.49 4-67.78  
RP LP CP RS LS CS

120 E 6 +/- LP

Zin=384.34 4-56.67  
RP LP CP RS LS CS

1000 ■ RP

Zin=306.73 4-41.82  
RP LP CP RS LS CS

The input impedance is 306.73  $\Delta$  -41.82° ohms.

### “LADDR” Program Listing.

#### Program:

```
00 < 154-Byte Prgm >
01 LBL "LADDR"
02 XEQ "FQ?"
03 SF 00
04 CLX
05 ENTER
06 COMPLEX
07 STO "Zin"
08 CF 21
09 FS? 55
10 SF 21

11 CLMENU
12 LBL A
13 "RP"
14 KEY 1 XEQ 01
15 "LP"
16 KEY 2 XEQ 02
17 "CP"
18 KEY 3 XEQ 03

19 FS? 00
20 GTO B
21 "RS"
22 KEY 4 XEQ 04
23 "LS"
24 KEY 5 XEQ 05
25 "CS"

26 KEY 6 XEQ 06
```

#### Comments:

Inputs the frequency using the “FQ?” utility on page 149.

Sets flag 00 (until the first element is entered).

Initializes  $Z_{in}$  and sets or clears flag 21 to match flag 55.

Defines the menu keys for entering elements in parallel.

If flag 00 is clear, declares the menu keys for entering elements in series.

Decodes the element location into two mesh or node numbers in the X- and Y-registers.

27 LBL B	Displays the menu and the input impedance. (If you want the impedance displayed in rectangular mode, you can change line 29 to 29 RECT and delete line 31.)
28 MENU	
29 POLAR	
30 VIEW "Zin"	
31 RECT	
32 STOP	
33 GTO A	
34 LBL 01	Converts a resistance to admittance.
35 1/X	
36 GTO 07	
37 LBL 02	Converts an inductance to admittance using the "C→Z" utility on page 148.
38 XEQ "C→Z"	
39 GTO 07	
40 LBL 03	Converts a capacitance to admittance using the "L→Z" utility on page 148.
41 XEQ "L→Z"	
42 LBL 07	Adds a parallel element.
43 RCL "Zin"	
44 FC?C 00	
45 1/X	
46 +	
47 1/X	
48 STO "Zin"	
49 RTN	
50 LBL 06	Converts a capacitance to impedance.
51 XEQ "C→Z"	
52 GTO 04	
53 LBL 05	Converts an inductance to impedance.
54 XEQ "L→Z"	
55 LBL 04	Adds a series element.
56 STO+ "Zin"	
57 END	

## Filter Design

---


This chapter contains programs for calculating component values for standard active filters and for Butterworth filters between equal terminations.

---

## Active Filter Design (“AF”)

This program calculates element values for the standard active filter circuits shown below. You must provide  $F$  (the corner or center frequency),  $G$  (the midband gain),  $PF$  or  $\alpha$  (the peaking factor), and  $C$  (a capacitor). The program then displays (and optionally prints) the list of elements that form the desired filter.

### Low Pass Filter.

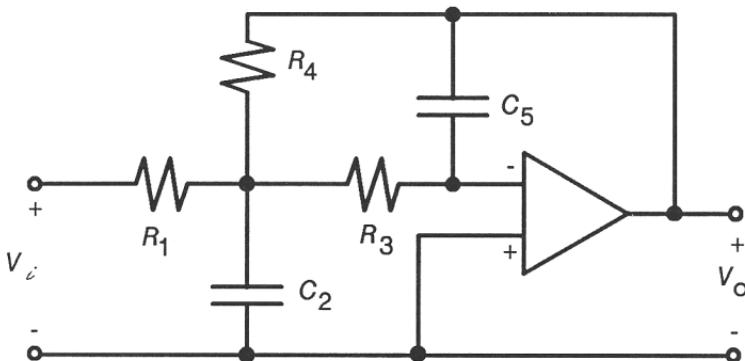

$$C_5 = C$$


$$C_2 = \frac{4C(G + 1)}{PF^2}$$

$$R_1 = \frac{PF}{4G\pi f_0 C}$$

$$R_3 = \frac{PF}{4\pi f_0 C (G + 1)} = \frac{G}{G + 1} R_1$$

$$R_4 = GR_1$$

## High Pass Filter.

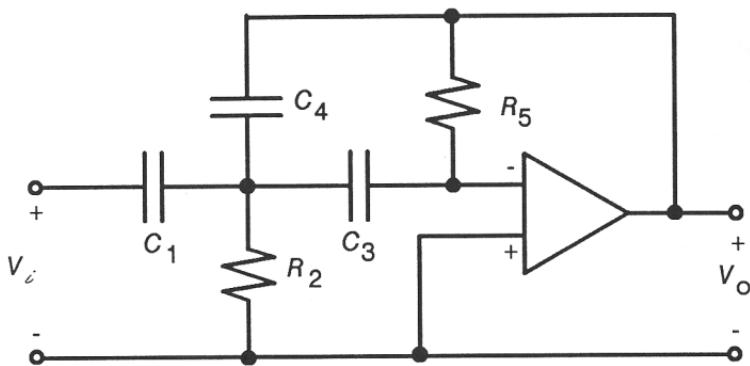


$$C_1 = C_3 = C$$

$$C_4 = \frac{C}{G}$$

$$R_2 = \frac{PF}{2\pi f_0 C \left( 2 + \frac{1}{G} \right)}$$

$$R_5 = \frac{2G + 1}{PF 2\pi f_0 C}$$

## Bandpass Filter.

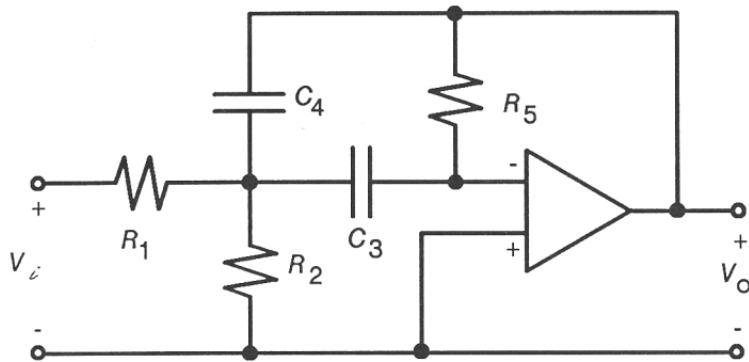

$$C_3 = C_4 = C$$

$$R_1 = \frac{1}{G 2\pi f_0 C PF}$$

$$R_2 = \frac{1}{\left( \frac{2}{PF^2} - G \right) 2\pi f_0 C PF}$$

$$R_5 = \frac{2}{PF 2\pi f_0 C}$$

## Variables Used.

In Equations	Description	In Program
$f_0$	Center frequency (Hz).	F
$G$	Midband gain (db).	G
$PF$	Peaking factor.	PF
$C$	Capacitor (farads).	C

**Remarks.** Flag 21 (*printer enable*) is set by the program.

## Program Instructions.

1. Key the “AF” program (listed on page 78) into your calculator.
2. Press **XEQ** **AF** (to run the “AF” program).
3. Press **INPUT**. The calculator prompts for  $F$ ,  $G$ ,  $PF$ , and  $C$ .
  - a. Key in a frequency,  $F$ , in Hertz; press **R/S**.
  - b. Key in the midband gain,  $G$ ; press **R/S**.
  - c. Key in a peaking factor,  $PF$ ; press **R/S**.
  - d. Key in a capacitance,  $C$ , in Farads; press **R/S**.

After entering these values, the program returns to the main menu.

4. Press **LOWP** (low pass), **HIGHP** (high pass), or **BAND** (band pass) to calculate the elements needed to build the particular filter.
5. When all of the elements have been displayed, press **R/S** to return to the main menu. Then go to step 3 to work another problem or press **EXIT** to quit.

**Example.** Design a high-pass active filter with the following characteristics:  $F = 10$  Hz,  $G = 10$ ,  $PF = 1$ , and  $C = 1 \mu\text{F}$ .

Select the ENG 3 display format and run the “AF” program.

**DISP** **ENG** 03 **XEQ** **AF**

x: 0.000E0  
**LOWP** **HIGHP** **BAND** **INPUT**

INPUT

Y: 0.000E0  
F?0.000E0

10 [R/S]

Y: 10.00E0  
G?0.000E0

10 [R/S]

Y: 10.00E0  
PF?0.000E0

1 [R/S]

Y: 1.000E0  
C?0.000E0

[E] 6 [+/-] [R/S]

x: 1.000E-6  
LOWP HIGHP BAND INPUT

HIGHP

R2=  
x: 7.579E3

If you're not using a printer, press [R/S] after each result.

[R/S]

R5=  
x: 334.2E3

[R/S]

C1=C3=C=  
x: 1.000E-6

[R/S]

C4=  
x: 100.0E-9

[R/S]

x: 100.0E-9  
LOWP HIGHP BAND INPUT

## “AF” Program Listing.

### Program:

```
00 C 309-Byte Prgm
01 LBL "AF"
02 SF 21
03 CLMENU
04 "LOWP"
05 KEY 1 XEQ A
06 "HIGHP"
07 KEY 2 XEQ B
08 "BAND"
09 KEY 3 XEQ C
10 "INPUT"
11 KEY 6 XEQ I
12 KEY 9 GTO 09

13 LBL 00
14 CLD
15 MENU
16 STOP
17 GTO 00

18 LBL A
19 "R1"
20 RCL "PF"
21 4
22 RCLX "G"
23 XEQ 04
24 ÷
25 XEQ 08
26 "R3"
27 RCLX "G"
28 ENTER
29 ENTER
30 LASTX
31 1
32 +
33 ÷
34 XEQ 08
```

### Comments:

Defines the menu for selecting a filter type.

Clears any message that may be displayed, displays the menu and stops. Pressing [R/S] redisplays the menu.

Calculates the elements for a low pass filter.

```
35 "R4"  
36 R+  
37 XEQ 08  
38 "C2"  
39 1  
40 RCL "G"  
41 RCLX "C"  
42 4  
43 ×  
44 RCL "PF"  
45 X†2  
46 ÷  
47 XEQ 08  
48 "C5=C"  
49 LBL 10  
50 RCL "C"  
51 GTO 08  
  
52 LBL B  
53 "R2"  
54 2  
55 XEQ 04  
56 RCL "G"  
57 1/X  
58 2  
59 +  
60 ×  
61 RCL÷ "PF"  
62 1/X  
63 XEQ 08  
64 "R5"  
65 2  
66 RCLX "G"  
67 1  
68 +  
69 2  
70 XEQ 04  
71 RCLX "PF"  
72 ÷  
73 XEQ 08  
74 "C1=C3=C"
```

Calculates the elements for a high pass filter.

```
75 XEQ 10
76 "C4"
77 RCL÷ "G"
78 GTO 08
79 LBL C
80 "R1"
81 2
82 XEQ 04
83 RCL× "G"
84 ENTER
85 ENTER
86 RCL× "G"
87 1/X
88 XEQ 08
89 "R2"
90 CLX
91 2
92 RCL "PF"
93 X↑2
94 ÷
95 RCL- "G"
96 ×
97 1/X
98 XEQ 08
99 "R5"
100 CLX
101 2
102 X<>Y
103 ÷
104 XEQ 08
105 "C3=C4=C"
106 GTO 10
107 LBL 04
108 PI
109 RCL× "F"
110 RCL× "C"
111 ×
112 RTN
```

Calculates the elements for a band pass filter.

Calculates  $\pi FC$ .

113 LBL I	Exits all menus and inputs <i>F</i> , <i>G</i> , <i>PF</i> , and <i>C</i> .
114 EXITALL	
115 INPUT "F"	
116 INPUT "G"	
117 INPUT "PF"	
118 INPUT "C"	
119 RTN	
120 LBL 08	Exits all menus. If results are being printed (flag 55 set), puts label and value on the same line.
121 EXITALL	
122 ←"="	
123 FS? 55	
124 ARCL ST X	
125 AVIEW	
126 LBL 09	Ends program.
127 END	

## Butterworth Filter Design (“BF”)

This program calculates component values for Butterworth filters between *equal* terminations. Inputs are termination resistance, passband characteristics, and attenuation at some out-of-band frequency.

Before the filter elements can be calculated, a normalized frequency must be computed from the desired cutoff or center frequency and passband characteristics. The normalized frequency is computed by one of these formulas:

Low Pass

$$\omega_n = \frac{\omega}{\omega_0}$$

High Pass

$$\omega_n = \frac{\omega_0}{\omega}$$


Band Pass

$$\omega_n = \frac{\omega^2 - \omega_0^2}{BW\omega}$$

Band Elimination

$$\omega_n = \frac{BW\omega}{\omega_0^2 - \omega^2}$$

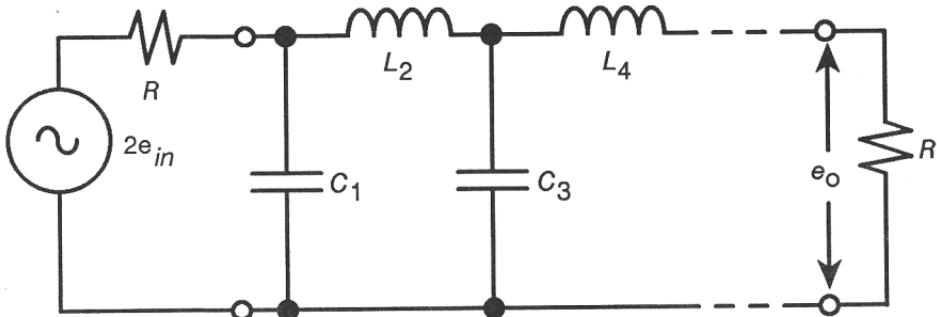The basic form of the filter is this *low-pass* prototype:



whose elements are given by the following set of formulas:

$$C_i = \frac{1}{\pi f_c R} \sin \frac{(2i - 1)\pi}{2n}, \quad i = 1, 3, 5, \dots, n - 1$$

$$L_i = \frac{R}{\pi f_c} \sin \frac{(2i - 1)\pi}{2n}, \quad i = 2, 4, 6, \dots, n$$

where:


$$n = INT \left[ \frac{1 + \ln(2 \times 10^{-\Delta dB/10} - 1)}{2 \ln(\omega / \omega_0)} \right]$$

Once the low-pass values have been calculated, if another passband characteristic is desired, the filter components are changed by one of the frequency transformations shown on the next page.


## Passband Characteristic

## Circuit Elements

Low pass

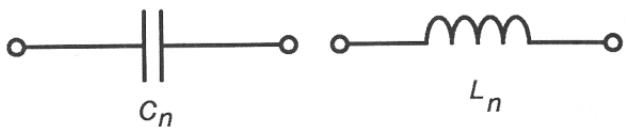


High pass

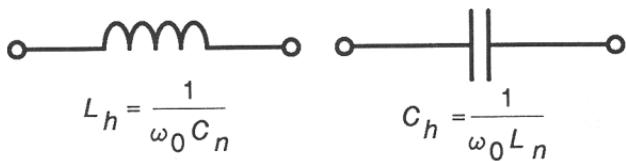


$$C_h = \frac{1}{\omega_0 L_n}$$

Band pass

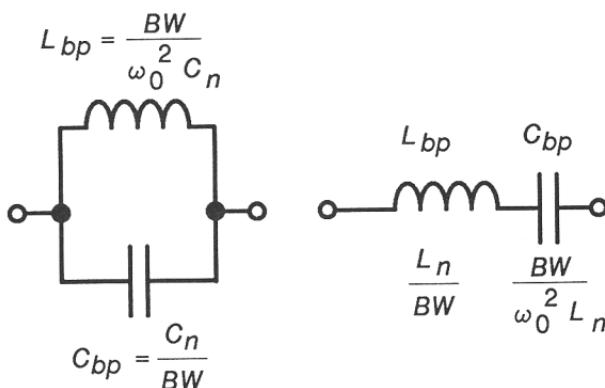

$$\frac{L_n}{BW} \quad \frac{BW}{\omega_0^2 L_n}$$

Band elimination

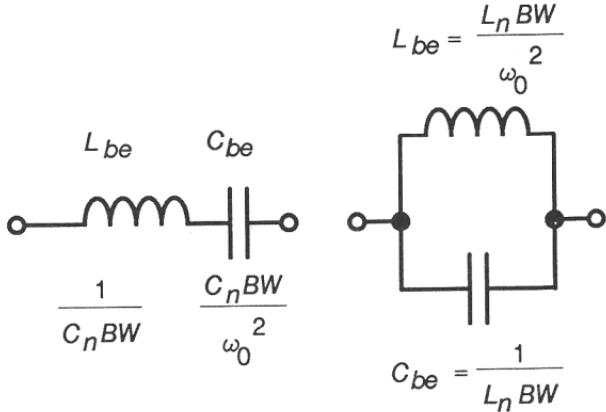

## Variables and Storage Registers Used.

In Equations	Description	In Program
$R$	Resistor (ohms).	R
$F_0$	Center frequency (Hz).	F0
$\omega_0$	Center frequency (radians/sec.).	R <sub>01</sub>
$F_1$	Attenuation frequency (Hz).	F1
	Amount of attenuation (dB).	A
$BW$	Band width (Hz).	BW
	Band width (radians/sec.).	R <sub>02</sub>
	Filter type (1-4).	R <sub>07</sub>
$n$	Filter order.	R <sub>09</sub>
$i$	Element counter.	R <sub>11</sub>

### Remarks.

- Flag 01 (set and cleared by the program) is used for branch control.
- Flag 21 (*printer enable*) is set by the program.
- Registers R<sub>08</sub>, R<sub>10</sub>, R<sub>13</sub>, and R<sub>14</sub> are used to store intermediate results. Be sure to set the SIZE to at least 15 registers ( MODES  SIZE 15 ).
- The “BF” program sets Radians mode.



#### Note

The program will give erroneous results if asked to calculate a filter order when  $A$  is small (when  $\Delta$ dB is close to Loss ( $\omega_0$ )).

## Program Instructions.

1. Key the “BF” program (listed on page 88) into your calculator.
2. Press **XEQ** **BF** (to run the “BF” the program).
3. The program displays a variable menu containing *R*, *F0*, *F1*, *A*, and *BW*. Store a value into each variable by keying in the value and then pressing the corresponding menu key.
4. After each of the five values has been stored, press **R/S**.
5. The program displays **Type?** and a menu containing the four types of filters. Press one of these keys to select a filter type:

**LOWP** (low pass)

**HIGHP** (high pass)

**BPASS** (band pass)

**BELIM** (band elimination)

6. The program then calculates and displays *N* and the filter elements. If you’re not using a printer, press **R/S** after each result is displayed.

**Example.** Design a 100-Hz wide Butterworth filter centered at 800 Hz with a 30-dB attenuation at 900 Hz.  $R_0$  is 50 ohms. The termination resistance, *R*, is also 50 ohms.

Select ENG 3 display format and run the “BF” program.

**DISP** **ENG** 03 **XEQ** **BF**

x: 0.000E0				
<b>R</b>	<b>F0</b>	<b>F1</b>	<b>A</b>	<b>BW</b>

Store the five inputs.

50 **R**

R=50.00E0				
<b>R</b>	<b>F0</b>	<b>F1</b>	<b>A</b>	<b>BW</b>

800 **F0**

F0=800.0E0				
<b>R</b>	<b>F0</b>	<b>F1</b>	<b>A</b>	<b>BW</b>

900 **F1**

F1=900.0E0				
<b>R</b>	<b>F0</b>	<b>F1</b>	<b>A</b>	<b>BW</b>

30 A

A=30.00E0				
R	F0	F1	A	BW

100 BW

BW=100.00E0				
R	F0	F1	A	BW

Continue with the program.

[R/S]

Type?			
LOWP	HIGHP	BPASS	SELIM

Select a band-pass filter. If you are not using a printer, press [R/S] after each result is displayed.

BPASS

N=
x: 6.000E0

[R/S]

C1=16.48E-6
L1=2.402E-3

[R/S]

L2=112.5E-3
C2=351.7E-9

[R/S]

C3=61.49E-6
L3=643.6E-6

[R/S]

L4=153.7E-3
C4=257.5E-9


[R/S]

C5=45.02E-6
L5=879.2E-6

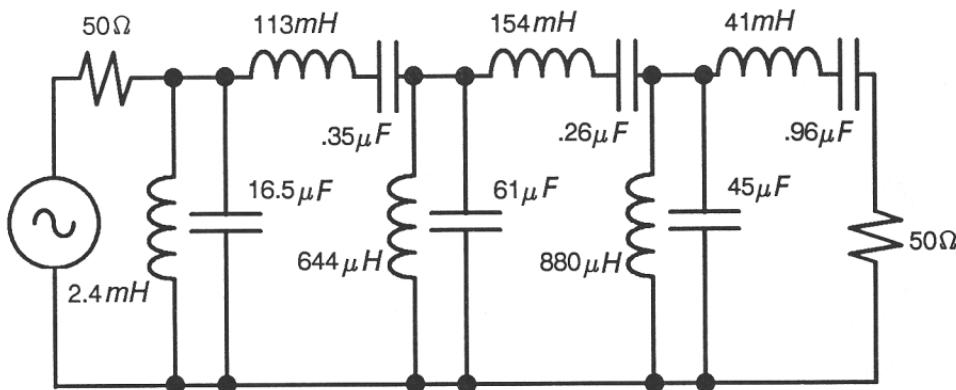**R/S**

$L_6=41.19 \times 10^{-3}$
$C_6=960.8 \times 10^{-9}$

Therefore, the filter you've calculated looks like this:



**“BF” Program Listing.** This program demonstrates that local labels do not have to be unique within a program as long as careful consideration is given to the local label search order (described in the owner’s manual).

**Program:**

```

00 C 394-Byte Prgm
01 LBL "BF"
02 MVAR "R"
03 MVAR "F0"
04 MVAR "F1"
05 MVAR "A"
06 MVAR "BW"
07 RAD

08 LBL A
09 VARMENU "BF"
10 CLA
11 STOP
12 ALENG
13 X#0?
14 GTO A

```

**Comments:**

01 LBL "BF"	Declares the menu variables and sets Radians mode.
08 LBL A	Displays the variable menu and stops. Pressing <b>R/S</b> is the only way to continue the program.

15 RCL "F0"	Converts the center frequency to radians/second.
16 XEQ 10	
17 STO 01	
18 CLMENU	Defines the menu for selecting a filter type. The <b>EXIT</b> key is defined to return to the variable menu.
19 "LOWP"	
20 KEY 1 GTO C	
21 "HIGHP"	
22 KEY 2 GTO D	
23 "BPASS"	
24 KEY 3 GTO E	
25 "BELIM"	
26 KEY 4 GTO F	
27 KEY 9 GTO A	
28 LBL B	Displays the menu and prompts for a filter type. Pressing <b>R/S</b> redisplays the menu.
29 MENU	
30 "Type?"	
31 PROMPT	
32 GTO B	
33 LBL C	Calculates the elements of a low pass filter (type 1).
34 1	
35 GTO 01	
36 LBL D	Calculates the elements of a high pass filter (type 2).
37 2	
38 GTO 01	
39 LBL E	Calculates the elements of a band pass filter (type 3).
40 3	
41 GTO 01	
42 LBL F	Calculates the elements of a band elimination filter (type 4).
43 4	
44 LBL 01	Exits all menus, stores the filter type, and sets flag 21 for proper output.
45 EXITALL	
46 STO 07	
47 SF 21	

```
48 RCL "BW"           Converts the band width to
49 XEQ 10             radians/second.
50 STO 02

51 LBL 00             Calculates the filter order.
52 RCL "F1"
53 RCL "A"
54 10
55 ÷
56 10↑X
57 2
58 ×
59 1
60 -
61 LN
62 STO 08
63 X<>Y
64 XEQ 10
65 XEQ 07
66 RCL 08
67 X<>Y
68 LN
69 ABS
70 ÷
71 1
72 +
73 2
74 ÷
75 IP
76 STO 09
77 STO 10

78 "N="
79 FS? 55           Displays the filter order. If results
80 R1P               are being printed (flag 55 set), the
81 AVIEW              label and result are displayed on the
82 ADV                same line.
83 LBL 08             Evaluates the Butterworth equations.
84 RCL 09
85 RCL- 10
```

```
86 1
87 +
88 STO 11
89 2
90 ×
91 1
92 -
93 PI
94 ×
95 2
96 ÷
97 RCL÷ 09
98 SIN
99 2
100 ×
101 LBL 09
102 STO 14
103 RCL "R"
104 -1
105 RCL 11
106 Y↑X
107 Y↑X
108 ×

109 GTO IND 07
110 LBL 01
111 RCL÷ 01
112 XEQ 06
113 GTO 00
114 LBL 02
115 RCL× 01
116 1/X
117 XEQ 06
118 +/--
119 GTO 00
120 LBL 03
121 SF 01
122 RCL÷ 02
123 XEQ 06
124 XEQ 00
125 ABS
```

Calculates the frequency transformation for the particular filter type.

126 1/X  
127 RCL 01  
128 X+2  
129 ÷  
130 XEQ 06  
131 +/-  
132 GTO 00  
133 LBL 04  
134 SF 01  
135 RCL $\times$  02  
136 RCL 01  
137 X+2  
138 ÷  
139 XEQ 06  
140 XEQ 00  
141 ABS  
142 RCL 01  
143 X+2  
144 ×  
145 1/X  
146 XEQ 06  
147 +/-  
148 LBL 00      Displays a pair of filter elements.  
149 FS? 01  
150 CLR  
151 X≥0?  
152 F" L"  
153 X<0?  
154 F" C"  
155 RCL 11  
156 AIP  
157 F" ="  
158 R+  
159 ABS  
160 ARCL ST X  
161 F" f"  
162 FC? 01  
163 AVIEW  
164 FS?C 01  
165 RTN

166 DSE 10	Repeats the Butterworth calculations for each element.
167 GTO 08	
168 RTN	
169 LBL 07	
170 STO 14	Calculates the normalized frequency for the particular filter type.
171 GTO IND 07	
172 LBL 04	
173 XEQ 03	
174 GTO 00	
175 LBL 02	
176 XEQ 01	
177 LBL 00	
178 1/X	
179 +/-	
180 GTO 05	
181 LBL 01	
182 RCL 14	
183 RCL $\div$ 01	
184 GTO 05	
185 LBL 03	
186 RCL 14	
187 X $\uparrow$ 2	
188 RCL 01	
189 X $\uparrow$ 2	
190 -	
191 RCL $\div$ 14	
192 RCL $\div$ 02	
193 LBL 05	
194 ABS	
195 STO 13	
196 RTN	
197 LBL 06	Multiplies by $-1^i$ .
198 -1	
199 RCL 11	
200 Y $\uparrow$ X	
201 X	
202 RTN	

203 LBL 10  
204 2  
205 X  
206 PI  
207 X  
208 END

Converts the frequency in the X-  
register (in Hz) to radians/second.

## Transmission Lines


---

This chapter contains programs that calculate the impedance of a lossy high-frequency transmission line and the high-frequency characteristic impedances for five types of transmission line configurations.


---
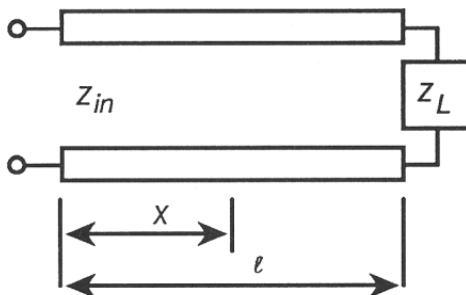
## Transmission Line Calculations (“LINE”)

This program calculates the input impedance of a lossy transmission line terminated in  $Z_L$ . The program provides an exact solution when the distributed line parameters  $R_0$  (defined as  $\sqrt{L \div C}$ ),  $R$ , and  $G$  are given. It provides an approximate solution when  $R_0$  and the conductor and dielectric losses are given.



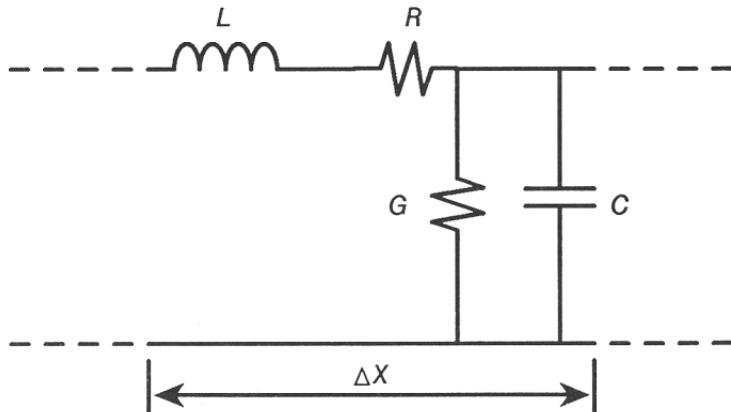The transmission line shown has a lumped model composed of elements  $L$ ,  $C$ ,  $R$ , and  $G$  as follows:



From this model the following equations can be derived:

$$R_0 = \sqrt{\frac{L}{C}}$$

$$r = \frac{R}{L} = \frac{v R}{R_0}$$

$$g = \frac{G}{C} = v R_0 G$$

where:

$L$  = inductance/unit length.

$C$  = capacitance/unit length.

$G$  = conductance/unit length.

$R$  = resistance/unit length.

$v = 3 \times 10^8 v_r$ .

$v_r$  = relative phase velocity.

$f$  = frequency, Hz.

$\omega = 2\pi f$  radians/second.

and

$$\alpha = \frac{1}{\sqrt{2v}} \left[ rg - \omega^2 + \sqrt{(r^2 + \omega^2)(g^2 + \omega^2)} \right]^{1/2}$$

$$\beta = \frac{1}{\sqrt{2v}} \left[ \omega^2 - rg + \sqrt{(r^2 + \omega^2)(g^2 + \omega^2)} \right]^{1/2}$$

The approximate solution is:

$$\operatorname{Re}\{Z_0\} = R_0 \left[ 1 + \frac{1}{2} \left( \frac{\alpha_C - \alpha_D}{\beta_0} \right) \left( \frac{3\alpha_D + \alpha_C}{\beta_0} \right) \right]$$

$$\operatorname{Im}\{Z_0\} = R_0 \left[ \frac{\alpha_D - \alpha_C}{\beta_0} \right]$$

$$\alpha = \alpha_C + \alpha_D$$

$$\beta = \beta_0 \left[ 1 + \frac{1}{2} \left( \frac{\alpha_C - \alpha_D}{\beta_0} \right)^2 \right]$$

where:

$\alpha_C$  = conductor loss, nepers/unit length =  $0.5(R/R_0)$

$\alpha_D$  = dielectric loss, nepers/unit length =  $0.5(GR)$

$$\beta_0 = \omega/v$$

Then

$$Z_{in} = Z_0 \left( \frac{1 + \Gamma_L e^{-2\gamma l}}{1 - \Gamma_L e^{-2\gamma l}} \right) \text{ ohms.}$$

where:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$l$  = line length

$Z_L$  = impedance of termination (ohms)

$Z_0$  = characteristic impedance of line =  $\operatorname{Re}\{Z_0\} + j \operatorname{Im}\{Z_0\}$  (ohms)

$\gamma$  = propagation constant of line =  $\alpha + j \beta$

$Z_0$  and  $\gamma$  are computed differently depending on which solution is selected.

$$\operatorname{Re}\{Z_0\} = \frac{R_0}{\sqrt{2(g^2 + \omega^2)}} \left[ rg + \omega^2 + \sqrt{(r^2 + \omega^2)(g^2 + \omega^2)} \right]^{1/2}$$

$$\operatorname{Im}\{Z_0\} = \frac{\pm R_0}{\sqrt{2(g^2 + \omega^2)}} \left[ -(rg + \omega^2) + \sqrt{(r^2 + \omega^2)(g^2 + \omega^2)} \right]^{1/2}$$

The + sign is chosen when  $g \geq r$  and the - sign is chosen when  $g < r$ .

### Variables Used.

In Equations	Description	In Program
$f$	Frequency.	f
$v_r$	Relative phase velocity.	vr
$R_0$	Characteristic impedance.	R0
$l$	Line length.	l
$Z_L$	Impedance of termination.	ZL

### Remarks.

- Flag 21 (*printer enable*) is set or cleared to match flag 55 (*printer existence*). This automatically produces printer output if flag 55 is set.
- Registers  $R_{00}$  thru  $R_{06}$  are used for storing intermediate results. Be sure to set the SIZE to at least seven registers (**MODES** ▼ **SIZE 7** **ENTER**) before running “LINE”.

### Program Instructions.

1. Key the “LINE” program (listed on page 102) into your calculator.
2. Select the desired angular and coordinate modes.
3. Press **[XEQ] LINE** (to run the “LINE” program). The program displays a variable menu containing  $f$ ,  $v_r$ ,  $R_0$ ,  $l$ , and  $Z_L$  (displayed as F, VR, R0, L, and ZL).
4. Store a value into each variable by keying in the value and pressing the corresponding menu key.

5. After all five variables have been stored, press **R/S**.
6. Select an exact or approximate solution.

For an exact solution:

- Press **EXACT**.
- The program prompts for *G*. Key in the conductance value and press **R/S**.
- The program then prompts for *R*. Key in the resistance value and press **R/S**.

For an approximate solution:

- Press **APPROX**.
- The program prompts for the conductor loss. Key in the value and press **R/S**.
- The program then prompts for the dielectric loss. Key in the value and press **R/S**.

- The value for  $Z_{in}$  is calculated and displayed. To calculate another solution, go to step 6. To work a new problem, press **EXIT** and go to step 4.

**Example.** A transmission line has the following properties:

$R = 1.2664$  ohms/cm.

$G = 0.00004187$  siemens/cm.

$R_0 = 55$  ohms.

$v_r = 0.85$ .

What is the input impedance of 3.5 cm of this line at 2 GHz if it is terminated in  $Z_L = 75 \angle -30^\circ$  ohms?

Select Degrees and Polar modes, select FIX 2 display format, and run the "LINE" program.

**MODES** DEG **MODES** POLAR  
**DISP** FIX 02 **XEQ** LINE

x: 0.00	F	VR	R0	L	ZL
---------	---	----	----	---	----

2 **E** 9 **F**

f=2,000,000,000.00	F	VR	R0	L	ZL
--------------------	---	----	----	---	----

.85 [VR]

V <sub>r</sub> =0.85				
F	VR	R <sub>0</sub>	L	Z <sub>L</sub>

55 [R<sub>0</sub>]

R <sub>0</sub> =55.00				
F	VR	R <sub>0</sub>	L	Z <sub>L</sub>

3.5 [L]

1=3.50				
F	VR	R <sub>0</sub>	L	Z <sub>L</sub>

75 [ENTER] 30 [+/-]  
[COMPLEX] Z<sub>L</sub>

Z <sub>L</sub> =75.00 ∠-30.00				
F	VR	R <sub>0</sub>	L	Z <sub>L</sub>

[R/S]

x: 2.75				
EXACT				APPROX

EXACT

y: 2.75				
G?0.00				

4.187 [E] 5 [+/-] [R/S]

y: 4.19E-5				
R?0.00				

1.2664 [R/S]

Z <sub>in</sub> =48.01 ∠28.48				
EXACT				APPROX

The required input impedance is 48.01 ∠28.48° ohms.

## **“LINE” Program Listing.**

### **Program:**

```
00 C 404-Byte Prgm
01 LBL "LINE"
02 MVAR "f"
03 MVAR "Vr"
04 MVAR "R0"
05 MVAR "1"
06 MVAR "ZL"
07 CF 21
08 FS? 55
09 SF 21

10 LBL A
11 CLA
12 VARMENU "LINE"
13 STOP
14 ALENG
15 X#0?
16 GTO A

17 RCL "f"
18 1E10
19 ÷
20 STO 04
21 2
22 PI
23 ×
24 ×
25 STO 03
26 RCL "1"
27 2
28 ×
29 3
30 RCL× "Vr"
31 STO 00
32 ÷
33 STO 02
```

### **Comments:**

Defines the menu variables and sets or clears flag 21 to match flag 55.

Displays the variable menu and stops. The program continues only when **[R/S]** is pressed.

Calculates intermediate results used by both solutions.

```
34 LBL B
35 CLMENU
36 "EXACT"
37 KEY 1 XEQ C
38 "APROX"
39 KEY 6 XEQ D
40 KEY 9 GTO A
41 MENU
42 STOP
43 GTO B
```

```
44 LBL C
45 EXITALL
46 INPUT "G"
47 INPUT "R"
48 RCLX 00
49 RCL÷ "R0"
50 STO 01
51 RCL "G"
52 RCLX "R0"
53 STOX 00
54 RCL 03
55 RCL 01
56 →POL
57 SQRT
58 STO 01
59 X<>Y
60 2
61 ÷
62 STO 06
63 RCL 03
64 RCL 00
65 →POL
66 SQRT
67 STO 00
68 X<>Y
69 2
70 ÷
71 STO 03
72 RCL+ 06
```

Displays a menu for selecting the type of solution. The **EXIT** key is defined to go back to the variable menu.

Calculates the “exact” solution.

```
73 STO 05
74 RCL 06
75 RCL- 03
76 STO "Vr"
77 RCL 01
78 RCL÷ 00
79 STO× "R0"
80 RCL 01
81 RCL× 00
82 STO× 02
83 GTO E

84 LBL D
85 EXITALL
86 CLMENU
87 "C loss?"
88 PROMPT
89 STO 00
90 "D loss?"
91 PROMPT
92 STO 03
93 RCL "1"
94 RCL "Vr"
95 RCL 04
96 PI
97 ×
98 1.5
99 ÷
100 X<>Y
101 ÷
102 STO 06
103 ×
104 2
105 ×
106 STO 02
107 RCL 03
108 10
109 LN
110 20
111 ÷

Calculates the "approximate" solution.
```

112 RCL÷ 06  
113 STO× 00  
114 STO× 03  
115 RCL 03  
116 RCL- 00  
117 ENTER  
118 STO 01  
119 RCL 03  
120 3  
121 ×  
122 RCL 00  
123 +  
124 ×  
125 2  
126 ÷  
127 +/-  
128 1  
129 +  
130 →POL  
131 STO× "R0"  
132 X<>Y  
133 STO "Vr"  
134 RCL 01  
135 X+2  
136 2  
137 ÷  
138 1  
139 +  
140 RCL 00  
141 RCL+ 03  
142 →POL  
143 STO× 02  
144 X<>Y  
145 STO 05

146 LBL E  
147 POLAR  
148 RCL "ZL"  
149 COMPLEX  
150 STO 06  
151 X<>Y  
152 STO 01  
153 RCL 05  
154 RCL 02  
155 →REC  
156 +/-  
157 E+X  
158 STO 02  
159 X<>Y  
160 180  
161 ×  
162 PI  
163 ÷  
164 STO 03  
165 RCL 06  
166 RCL- "Vr"  
167 RCL 01  
168 RCL÷ "R0"  
169 →REC  
170 1  
171 +  
172 →POL  
173 1/X  
174 -2  
175 ×  
176 X<>Y  
177 +/-  
178 X<>Y  
179 →REC  
180 1  
181 +  
182 →POL  
183 RCL× 02

Completes the calculations for both solutions.

```
184 1/X
185 X<>Y
186 RCL- 03
187 +/--
188 X<>Y
189 →REC
190 1
191 -
192 →POL
193 1/X
194 2
195 ×
196 X<>Y
197 +/--
198 X<>Y
199 →REC
200 1
201 +
202 →POL
203 RCL× "R0"
204 X<>Y
205 RCL "Vr"
206 +
207 COMPLEX
208 "Zin="
209 ARCL ST X
210 AVIEW
211 END
```

Displays the result and returns to the menu at LBL B.

---

## Transmission Line Impedance (“TLI”)

This program calculates the high frequency characteristic impedance ( $Z_0$ ) for five types of transmission lines:

Open two-wire line:

$$Z_0 = \frac{120}{\sqrt{\epsilon_r}} \ln \left( \frac{2D}{d} \right)$$

Single wire near ground:

$$Z_0 = \frac{138}{\sqrt{\epsilon_r}} \log \left( \frac{4h}{d} \right)$$

Balanced wires near ground:

$$Z_0 = \frac{276}{\sqrt{\epsilon_r}} \log \left\{ \frac{2D}{d} \left[ 1 + \left( \frac{D}{2h} \right)^2 \right]^{-1/2} \right\}$$

Wires in parallel near ground:

$$Z_0 = \frac{69}{\sqrt{\epsilon_r}} \log \left\{ \frac{4h}{d} \left[ 1 + \left( \frac{2h}{D} \right)^2 \right]^{+1/2} \right\}$$

Coaxial line:

$$Z_0 = \frac{60}{\sqrt{\epsilon_r}} \ln \frac{D}{d}$$

### Variables Used.

In Equations	Description	In Program
$D$	Wire spacing.	D
$d$	Wire diameter.	dia
$h$	Height of wire (above ground).	h
$\epsilon_r$	Relative permittivity.	e

**Remarks.** Flag 21 (*printer enable*) is set or cleared to match flag 55 (*printer existence*). This automatically produces printer output if flag 55 is set.

### Program Instructions.

1. Key the “TLI” program (listed on page 111) into your calculator.
2. Press **[XEQ] TLI** (to run the “TLI” program).
3. Use the variable menu displayed by the program to store the required inputs for the particular line configuration you’re working with.
4. Press **[R/S]**.
5. The program displays **Line Config?** and a menu containing the five types of line configurations. Select a configuration by pressing the corresponding menu key:

**OP** (open two-wire line)

**SW** (single wire near ground)

**B** (balanced wires near ground)

**P** (wires in parallel near ground)

**C** (coaxial line)

6. The value of  $Z_0$  is displayed and the program returns to the input menu (step 3).

**Example.** Calculate  $Z_0$  of RG-218/U coaxial cable with wire spacing,  $D = 0.68$  in., wire  $dia = 0.195$  in., and  $\epsilon_r$  of the polyethylene insulation = 2.3.

Select FIX 2 display format and run the “TLI” program.

**[DISP] FIX 02 [XEQ] TLI**

x: 0.00			
D	DIA	H	E

Store the inputs.

.68 **D**

D=0.68			
D	DIA	H	E

.195 DIA

dia=0.20

D	DIA	H	E		
---	-----	---	---	--	--

2.3 E

e=2.30

D	DIA	H	E		
---	-----	---	---	--	--

Calculate  $Z_0$  for the *coaxial* configuration.

R/S

Line Config?

DP	SW	B	P	C	
----	----	---	---	---	--

C

$Z_0=49.42$

D	DIA	H	E		
---	-----	---	---	--	--

Now calculate  $Z_0$  for an open two-wire (air) line with  $D = 6$  in. and  $dia = 0.0808$  in. ( $\epsilon_r$  of air = 1).

6 D

D=6.00

D	DIA	H	E		
---	-----	---	---	--	--

.0808 DIA

dia=0.08

D	DIA	H	E		
---	-----	---	---	--	--

1 E

e=1.00

D	DIA	H	E		
---	-----	---	---	--	--

R/S

Line Config?

DP	SW	B	P	C	
----	----	---	---	---	--

OP

$Z_0=600.08$

D	DIA	H	E		
---	-----	---	---	--	--

This time, calculate  $Z_0$  of an air line ( $\epsilon_r$  of air = 1) consisting of a single 0.1285 inch diameter wire 6 inches from a ground plane.

.1285 DIA

dia=0.13

D	DIA	H	E		
---	-----	---	---	--	--

6 H

h=6.00

D	DIA	H	E		
---	-----	---	---	--	--

1 E

e=1.00

D	DIA	H	E		
---	-----	---	---	--	--

R/S

Line Config?

DP	SW	B	P	C	
----	----	---	---	---	--

SW

Z0=313.44

D	DIA	H	E		
---	-----	---	---	--	--

## "TLI" Program Listing.

### Program:

```
00 C 225-Byte Progm
01 LBL "TLI"
02 MVAR "D"
03 MVAR "dia"
04 MVAR "h"
05 MVAR "e"
06 CF 21
07 FS? 55
08 SF 21
```

### Comments:

Declares menu variables and sets or  
clears flag 21 to match flag 55.

```
09 LBL A
10 VARMENU "TLI"
11 CLA
12 STOP
13 ALENG
14 X#0?
15 GTO A

16 CLMENU
17 "OP"
18 KEY 1 XEQ 01
19 "SW"
20 KEY 2 XEQ 02
21 "B"
22 KEY 3 XEQ 03
23 "P"
24 KEY 4 XEQ 04
25 "C"
26 KEY 5 XEQ 05
27 KEY 9 GTO A

28 MENU
29 "Line Config?"
30 PROMPT
31 GTO A

32 LBL 01
33 XEQ 07
34 LN
35 120
36 GTO 06

37 LBL 02
38 XEQ 08
39 LOG
40 138
41 GTO 06
```

Displays the variable menu and stops.

Defines the programmable menu for the five configurations. The **EXIT** key is defined to return to the variable menu.

Displays the menu and prompts for a selection. After the appropriate routine is executed, returns to the variable menu.

Calculates  $Z_0$  for an open two-wire configuration.

Calculates  $Z_0$  for a single wire near the ground.

```
42 LBL 03          Calculates  $Z_0$  for balanced wires
43 XEQ 09          near the ground.
44 1/X
45 1
46 +
47 SQRT
48 1/X
49 XEQ 07
50 x
51 LOG
52 276
53 GTO 06

54 LBL 04          Calculates  $Z_0$  for wires in parallel
55 XEQ 09          near the ground.
56 1
57 +
58 XEQ 08
59 SQRT
60 XEQ 08
61 x
62 LOG
63 69
64 GTO 06

65 LBL 05          Calculates  $Z_0$  for a coaxial line
66 RCL "D"          configuration.
67 RCL÷ "dia"
68 LN
69 60

70 LBL 06          Completes the calculation and
71 RCL "e"          displays the result.
72 SQRT
73 ÷
74 x
75 "Z0="
76 ARCL ST X
77 AVIEW
78 RTN
```

```
79 LBL 07          Calculates an intermediate result.
80 2
81 RCLx "D"
82 RCL÷ "dia"
83 RTN

84 LBL 08          Calculates an intermediate result.
85 4
86 RCLx "h"
87 RCL÷ "dia"
88 RTN

89 LBL 09          Calculates an intermediate result.
90 2
91 RCLx "h"
92 RCL÷ "D"
93 X2
94 END
```


## Amplifier Analysis

---

This chapter contains programs that calculate small-signal properties of a transistor amplifier and automate a method of transistor bias optimization.
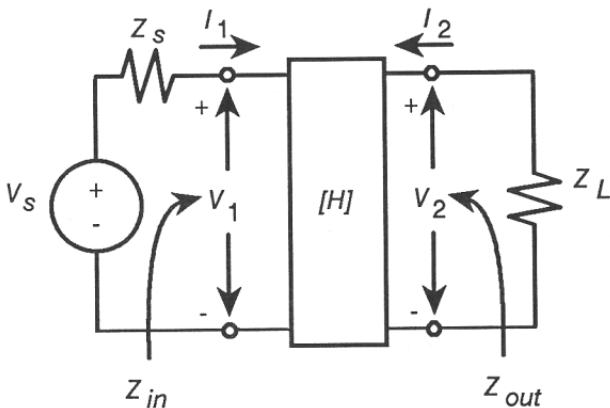
## Transistor Amplifier Performance (“TAP”)

This program calculates certain small-signal properties of a transistor amplifier given the  $h$ -parameter matrix and the source and load impedances. The program calculates current and voltage gains, and input and output impedances.



**Equations.** The definition of the  $h$ -parameter matrix is:

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_i & h_r \\ h_f & h_o \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

The current gain is:

$$A_i = \frac{i_2}{i_1} = \frac{-h_f}{1 + h_o Z_L}$$

The voltage gain is:

$$A_v = \frac{v_2}{v_1} = \frac{A_i Z_L}{Z_{in}}$$

The voltage gain with a source resistor is:

$$A_{vs} = \frac{v_2}{v_s} = \frac{A_i Z_L}{Z_{in} + Z_s}$$

The input impedance is:

$$Z_{in} = h_i + h_r Z_L A_i$$

The output impedance is:

$$Z_{out} = \frac{h_i + Z_S}{h_o h_i + h_o Z_S - h_f h_r}$$

## Variables Used.

In Equations	Description	In Program
$h_i$	Matrix h-parameter.	hi
$h_r$	Matrix h-parameter.	hr
$h_f$	Matrix h-parameter.	hf
$h_o$	Matrix h-parameter.	ho
$Z_S$	Source impedance.	zs
$Z_L$	Load impedance.	z1

**Remarks.** Flag 21 (*printer enable*) is set or cleared to match flag 55 (*printer existence*). This automatically produces printer output if flag 55 is set.

## Program Instructions.

1. Key the “TAP” program (listed on page 120) into your calculator.
2. Press **[XEQ] TAP** (to run the “TAP” program).
3. Use the variable menu displayed by the program to store the four h-parameter values ( $h_i$ ,  $h_r$ ,  $h_f$ , and  $h_o$ ) and the source and load impedances ( $Z_S$  and  $Z_L$ ).
4. Press **[R/S]** to display the result menu.
5. Press the appropriate menu key for each result you want to calculate:
  - **[F1]** to display the current gain,  $A_i$ .
  - **[F2]** to display the voltage gain,  $A_v$ .

- **AVS** to display the voltage gain with a source resistor,  $A_{vs}$ .
- **ZIN** to display the input impedance,  $Z_{in}$ .
- **ZOUT** to display the output impedance,  $Z_{out}$ .

6. Press **EXIT** to return to the variable menu (step 3).

**Example.** What are the small-signal properties of a transistor that has the following h-parameter matrix and has source and load impedances of 1,000 and 10,000 ohms, respectively?


$$h = \begin{bmatrix} 1100 & 250E-6 \\ 50 & 25E-6 \end{bmatrix}$$

Select the FIX 4 display format and run the “TAP” program.

**DISP FIX 04 XEQ TAP** 

Using the variable menu, enter each of the six input values and then press **R/S**.


1100 **HI**

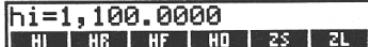

250 **E 6 +/- HR**



50 **HF**

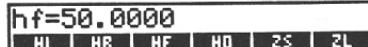

25 **E 6 +/- HO**



1000 **ZS**



10000 ZL

Z1=10,000.0000					
HI	HR	HF	HO	ZS	ZL

R/S

x: 0.0000					
HI	AV	AVS	ZIN	ZOUT	

For each of the outputs you want to calculate, press the corresponding menu key.

AI

Ai=-40.0000					
HI	AV	AVS	ZIN	ZOUT	

AV

Av=-400.0000					
HI	AV	AVS	ZIN	ZOUT	

AVS

Avs=-200.0000					
HI	AV	AVS	ZIN	ZOUT	

ZIN

Zin=1,000.0000					
HI	AV	AVS	ZIN	ZOUT	

ZOUT

Zout=52,500.0000					
HI	AV	AVS	ZIN	ZOUT	

Press **EXIT** to return to the input menu.

**EXIT**

x: 52,500.0000					
HI	HR	HF	HO	ZS	ZL

From here you can work another problem or press **EXIT** again to quit.

## “TAP” Program Listing.

### Program:

```
00 < 227-Byte Prgm >
01 LBL "TAP"
02 MVAR "hi"
03 MVAR "hr"
04 MVAR "hf"
05 MVAR "ho"
06 MVAR "Zs"
07 MVAR "Z1"
08 CF 21
09 FS? 55
10 SF 21

11 LBL A
12 VARMENU "TAP"
13 CLA
14 STOP
15 ALENG
16 X#0?
17 GTO A

18 CLMENU
19 "Ai"
20 KEY 1 XEQ 01
21 "Av"
22 KEY 2 XEQ 02
23 "Avs"
24 KEY 3 XEQ 03
25 "Zin"
26 KEY 4 XEQ 04
27 "Zout"
28 KEY 5 XEQ 05
29 KEY 9 GTO A

30 LBL 00
31 MENU
32 STOP
33 GTO 00
```

### Comments:

Declares the menu variables and sets or clears flag 21 to match flag 55.

Displays the variable menu and stops.

Defines the programmable menu for displaying the results. The **EXIT** key is defined to return to the variable menu.

Displays the programmable menu and stops. The menu is redisplayed after each result.

34 LBL 01	Calculates $A_i$ .
35 XEQ 07	
36 "Ai"	
37 GTO 06	
38 LBL 02	Calculates $A_v$ .
39 XEQ 08	
40 ÷	
41 "Av"	
42 GTO 06	
43 LBL 03	Calculates $A_{vs}$ .
44 XEQ 08	
45 RCL+ "Zs"	
46 ÷	
47 "Avs"	
48 GTO 06	
49 LBL 04	Calculates $Z_{in}$ .
50 XEQ 08	
51 "Zin"	
52 GTO 06	
53 LBL 05	Calculates $Z_{out}$ .
54 RCL "hi"	
55 RCL+ "Zs"	
56 LASTX	
57 RCL "ho"	
58 ×	
59 LASTX	
60 RCL× "Zs"	
61 +	
62 RCL "hf"	
63 RCL× "hr"	
64 -	
65 ÷	
66 "Zout."	

```

67 LBL 06
68 ↑ "="
69 ARCL ST X
70 AVIEW
71 RTN

72 LBL 07
73 RCL "hf"
74 +/-  

75 1
76 RCL "ho"
77 RCL $\times$  "Z1"
78 +
79 ÷
80 RTN

81 LBL 08
82 XEQ 07
83 RCL $\times$  "Z1"
84 ENTER
85 RCL $\times$  "hr"
86 RCL+ "hi"
87 END

```

Displays a result.


Calculates  $A_i$ .

Calculates  $Z_{in}$ .

---
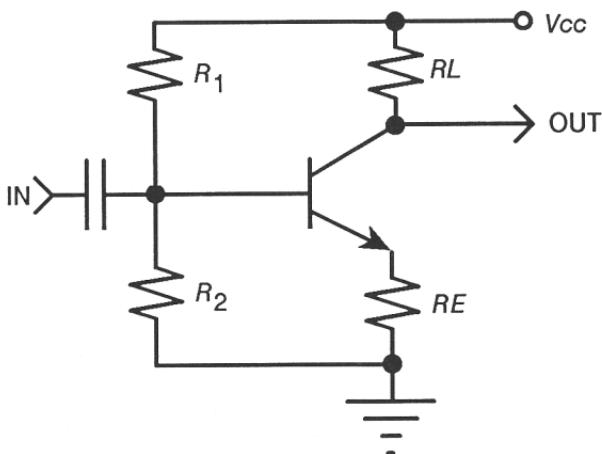
## Transistor Amplifier Bias Optimization (“BIAS”)

This program automates the method of bias optimization described in “Designing Class ‘A’ Amplifiers to Meet Specified Tolerances,” by Ward J. Helms (*Electronics*, August 8, 1974). The program requires you to specify a set of parameters from which it determines, by an iterative technique, the optimum values for  $R_1$ ,  $R_2$ ,  $R_E$ , and  $R_L$ . The minimum power gain is also computed.



**How “BIAS” Works.** First, values are input for the variables listed in the table on page 126. Then, the transistor’s thermal resistance is calculated:

$$\theta_{JA} = (T_{\max} - 25^\circ C) / P_D$$

and the minimum load resistance and emitter resistance are estimated:

$$R_{L1} = \frac{\theta_{JA} V_{CC}^2}{4.4 (T_{J\max} - T_{A\max})} = R_{Ln}$$

$$R_{E1} = 0.1 R_{L1} = R_{En}$$

Next, the quiescent, maximum, and minimum collector currents are calculated:

$$I_{CQ} = \frac{V_{CC}}{2(R_{Ln} + R_{En})}$$

$$I_{C\max} = I_{CQ} (1 + \Delta I_{CQ})$$

$$I_{C\min} = I_{CQ} (1 - \Delta I_{CQ})$$

From these, we can calculate the base-emitter voltage under hot, high-current conditions ( $V_{BEX}$ ) and under cold, low-current conditions ( $V_{BEN}$ ).

$$T_{\max} = \theta_{JA} I_{CQ} (V_{CC}/2) + T_{A\max}$$

$$V_{BEX} = V_{BE1\min} + \Delta V_{BE} \log(I_{C\max}/I_1) - 0.0022(T_{\max} - 25^\circ C)$$

$$T_{\min} = \theta_{JA} I_{CQ} (V_{CC}/2) (1 - (\Delta I_{CQ})^2) + T_{A\min}$$

$$V_{BEN} = V_{BE1\max} + \Delta V_{BE} \log(I_{C\min}/I_1) - 0.0022(T_{\min} - 25^\circ C)$$

Now, a better estimate of the emitter resistance can be made:

$$R_{E(n+1)} = \frac{-2(V_{BEX} - V_{BEN})}{I_{C\max} - I_{C\min}}$$

From this point, if  $V_{BEX} > V_{BEN}$ , then  $R_E$  is set to zero,  $R_L$  is increased by 10% and the design procedure is repeated. Iterations continue until

$$\frac{R_{E(n+1)} - R_{En}}{R_{En}} < 0.5\%$$

If at any time the condition  $T_{\max} > T_{J\max}$  occurs,  $R_L$  is increased by 10%.

When the iterative procedure is complete,  $T_{\max}$ ,  $I_{C\max}$ ,  $T_{\min}$ , and  $I_{C\min}$  are displayed.

Values for

$h_{FE \max}$  = maximum worst-case current gain at  $T_{\max}$  or  $T_{\min}$  and  $I_C \max$  or  $I_C \min$

and

$h_{FE \min}$  = minimum worst-case current gain at  $T_{\max}$  or  $T_{\min}$  and  $I_C \max$  or  $I_C \min$

are determined from the transistor's data sheet. The Thevenin-equivalent resistance ( $R_B$ ) and voltage ( $V_{BB}$ ) of the amplifier's bias network are calculated:

$$R_B = \frac{h_{FE \max} h_{FE \min} \left[ R_{E(n+1)} (I_C \max - I_C \min) + V_{BEX} - V_{BEN} \right]}{h_{FE \max} I_C \min - h_{FE \min} I_C \max}$$

$$V_{BB} = V_{BEN} + I_C \min \left( \left( R_B / h_{FE \min} \right) + R_{E(n+1)} \right)$$

Now the bias resistors are calculated:

$$R_1 = \frac{R_B V_{CC}}{V_{BB}}$$

$$R_2 = \frac{R_B V_{CC}}{V_{CC} - V_{BB}}$$

Finally, the minimum power gain and minimum signal power are calculated:

$$A_P = \frac{R_B R_L h_{FE \min}}{R_E (R_B + h_{FE \min} R_E)}$$

$$P_S = (1 - \Delta I_{CQ})^2 \left( \frac{V_{CC}^2 R_L}{8(R_L + R_E)^2} \right)$$

## Variables Used.

In Equations	Description	In Program
$V_{CC}$	Source voltage (volts).	VCC
$\Delta I_{CQ}$	Maximum desired percentage variation of quiescent current.	dICQ
$T_A \text{ max}$	Maximum ambient temperature (use the maximum case temperature for a transistor mounted on a heat sink).	TAmax
$T_A \text{ min}$	Minimum ambient temperature.	TAmin
$T_J \text{ max}$	Maximum junction temperature.	TJmax
$P_D$	Maximum rated power dissipation at 25°C.	PD
$I_1$	Collector current, usually selected for convenience so that $I_1$ and $10 I_1$ at 25°C bracket the expected operating point.	I1
$\Delta V_{BE}$	Typical base-emitter voltage change over the range of $I_1$ to $10 I_1$ at 25°C.	dVBE
$V_{BE1 \text{ min}}$	Minimum base-emitter voltage at $I_1$ at 25°C.	VBE1min
$V_{BE1 \text{ max}}$	Maximum base-emitter voltage at $I_1$ at 25°C.	VBE1max
$h_{FE \text{ max}}$	Maximum worst-case current gain at $T_{\text{max}}$ or $T_{\text{min}}$ and $I_{C \text{ max}}$ or $I_{C \text{ min}}$ .	R01
$h_{FE \text{ min}}$	Minimum worst-case current gain at $T_{\text{max}}$ or $T_{\text{min}}$ and $I_{C \text{ max}}$ or $I_{C \text{ min}}$ .	R02

## Remarks.

- Flag 01 is used for branching control.
- Flag 02 is used to control the labels given to results.
- Flag 21 (*printer enable*) and flag 55 (*printer existence*) control printer output.
- Registers R<sub>00</sub> through R<sub>09</sub> are used for storing intermediate results. Be sure to set the SIZE to at least 10 registers (■ MODES ▼ SIZE 10 [ENTER]) before running "BIAS".

## Program Instructions.

1. Key the "BIAS" program (listed on page 130) into your calculator.
2. Press [XEQ] BIAS (to run the "BIAS" program).
3. Input the variables as prompted; press [R/S] after each entry.
4. After the last input, the program calculates and displays  $T_{\max}$  and  $I_{\max}$ . The program then calculates and displays  $T_{\min}$  and  $I_{\min}$ .
5. When you see  $H_{\max}?$ , key in a value for the maximum worst-case current gain at  $T_{\max}$  or  $T_{\min}$  and  $I_{C\max}$  or  $I_{C\min}$ . Press [R/S].
6. When you see  $H_{\min}?$ , key in a value for the minimum worst-case current gain at  $T_{\max}$  or  $T_{\min}$  and  $I_{C\max}$  or  $I_{C\min}$ . Press [R/S].
7. The program then calculates values for  $R_E$ ,  $R_L$ ,  $R_1$ ,  $R_2$ , and  $A_P$ . If you are not using a printer, press [R/S] after each result is displayed.

**Example.** A single-stage class "A" amplifier is connected to a 30-volt power supply. Calculate the maximum power output and maximum power gain obtained from a transistor over an ambient temperature range of 0°C to 70°C, with a maximum quiescent-current variation of  $\pm 20\%$  (or .2).

From the transistor's data sheet,

$$T_{J\max} = 150^\circ\text{C}$$

$$PD = 0.36 \text{ W}$$

$$\Delta V_{BE} = 0.10 \text{ v from 3 to 30 mA}$$

$$V_{BE1\min} = 0.52 \text{ v at 3 mA at } 25^\circ\text{C}$$

$$V_{BE1\max} = 0.72 \text{ v at 3 mA at } 25^\circ\text{C}$$

$$I_1 = 0.001 \text{ A}$$

$$h_{FEmax} = 600$$

$$h_{FEmin} = 100$$

Select ENG 2 display format and run the “BIAS” program.

■ [DISP] ENG 02 [XEQ] BIAS

Y: 0.00E0  
VCC?0.00E0

30 [R/S]

Y: 30.0E0  
dICQ?0.00E0

.2 [R/S]

Y: 200.E-3  
TAmax?0.00E0

70 [R/S]

Y: 70.0E0  
TAmmin?0.00E0

0 [R/S]

Y: 0.00E0  
TJmax?0.00E0

150 [R/S]

Y: 150.E0  
PD?0.00E0

.36 [R/S]

Y: 360.E-3  
I1?0.00E0

.001 [R/S]

Y: 1.00E-3  
dVBE?0.00E0

.1 [R/S]

Y: 100.E-3  
VBE1min?0.00E0

.52 [R/S]

Y: 520.E-3  
VBE1max?0.00E0

.72 [R/S]

Tmax=148.E0  
I<sub>max</sub>=18.0E-3

[R/S]

Tmin=74.8E0  
I<sub>min</sub>=12.0E-3

[R/S]

Hmax?  
x: 500.E-3

Refer again to the transistor's data sheet and input  $h_{FEmax}$ .

600 [R/S]

Hmin?  
x: 600.E0

Now, input  $h_{FEmin}$ .

100 [R/S]

RE=  
x: 115.E0

[R/S]

RL=  
x: 888.E0

[R/S]

R2=  
x: 4.18E3

[R/S]

R1=  
x: 45.0E3

**R/S**

**AP=**  
**x: 22.9E0**

## **"BIAS" Program Listing.**

### **Program:**

```
00 < 553-Byte Prgm >
01 LBL "BIAS"
02 INPUT "VCC"
03 INPUT "dICQ"
04 INPUT "TAmax"
05 STO 07
06 INPUT "TAmin"
07 STO 08
08 INPUT "TJmax"
09 INPUT "PD"
10 STO 09
11 INPUT "I1"
12 INPUT "dVBE"
13 INPUT "VBE1min"
14 INPUT "VBE1max"

15 CF 01
16 SF 02
17 SF 21
18 RCL "TJmax"
19 25
20 -
21 RCL÷ 09
22 STO 09
23 RCL "VCC"
24 X†2
25 X
26 RCL "TJmax"
27 RCL- "TAmax"
28 4.4
29 X
30 ÷
```

### **Comments:**

Inputs values.

Initializes values for iterative process.

```
31 STO 03
32 0.1
33 ×
34 STO 04
35 LBL 00
36 RCL "VCC"
37 2
38 ÷
39 ENTER
40 ENTER
41 RCL 03
42 RCL+ 04
43 ÷
44 STO 00
45 RCL× 09
46 ×
47 RCL+ 07
48 RCL "TJmax"
49 X<>Y
50 X>Y?
51 GTO 05
52 XEQ 03
53 +/- 
54 RCL "dICQ"
55 1
56 +
57 XEQ 04
58 RCL+ "VBE1min"
59 STO 05
60 1
61 RCL "dICQ"
62 X†2
63 -
64 2
65 ÷
66 RCL× 00
67 RCL× 09
68 RCL× "VCC"
69 RCL+ 08
70 XEQ 03
Begins iterative loop.
```

```

71 +/-  

72 1  

73 RCL- "dICQ"  

74 XEQ 04  

75 RCL+ "VBE1max"  

76 STO 06  

77 RCL 05  

78 X>Y?  

79 GTO 02  

80 -  

81 RCL÷ 00  

82 RCL÷ "dICQ"  

83 RCL 04  

84 X<>Y  

85 STO 04

86 %CH          Repeats iterative loop as needed.  

87 0.5  

88 X≤Y?  

89 GTO 00  

90 FS? 01  

91 GTO 01  

92 SF 01  

93 GTO 00

94LBL 01          Prompts for  $h_{FEmax}$  and  $h_{FEmin}$ .  

95 CF 01  

96 "Hmax?"  

97 PROMPT  

98 STO 01  

99 "Hmin?"  

100 PROMPT  

101 STO 02

102 X<>Y          Calculates  $R_B$ .  

103 RCL "dICQ"  

104 2  

105 x  

106 RCLx 00  

107 RCLx 04  

108 RCL+ 05

```

```

109 RCL- 06
110 RCL× 02
111 RCL× 01
112 1
113 RCL- "dICQ"
114 RCL× 01
115 1
116 RCL+ "dICQ"
117 RCL× 02
118 -
119 ÷
120 RCL÷ 00
121 STO 07

122 RCL÷ 02
123 RCL+ 04
124 RCL× 00
125 1
126 RCL- "dICQ"
127 ×
128 RCL+ 06
129 STO 08

130 RCL "VCC"
131 X<>Y
132 ÷
133 RCL× 07
134 RCL "VCC"
135 RCL× 07
136 LASTX
137 RCL- 08
138 ÷

139 RCL 03
140 RCL 04
141 "RE"
142 XEQ 02
143 "RL"
144 XEQ 02
145 "R2"
146 XEQ 02

```

Calculates  $V_{BB}$ .

Calculates  $R_1$ .

Calculates  $R_2$ .

Recalls  $R_L$  and  $R_E$ , and then displays each of the four values in the stack.

147 "R1"  
148 XEQ 02  
149 ÷  
150 RCL $\times$  02  
151 RCL 07  
152  $\times$   
153 LAST $\times$   
154 RCL 04  
155 RCL $\times$  02  
156 +  
157 ÷  
158 LOG  
159 10  
160  $\times$   
161 "AP"  
162 LBL 02  
163  $\leftarrow$ =""  
164 FS? 55  
165 ARCL ST X  
166 AVIEW  
167 R<sub>4</sub>  
168 RTN  
169 LBL 03  
170 FS? 01  
171 XEQ A  
172 25  
173 -  
174 2.2E-3  
175  $\times$   
176 RTN  
177 LBL A  
178 "T<sub>max</sub>="  
179 FC? 02  
180 "T<sub>min</sub>="  
181 ARCL ST X  
182  $\leftarrow$ "T"  
183 RTN

Calculates and then displays the power gain. (When the RTN at line 168 is reached, the program ends because there are no pending subroutine calls.)

Displays a result and rolls the stack down one register (for the next result).

Calculates temperature.

Displays proper label and temperature.

184 LBL 04	Calculates current.
185 RCL $\times$ 00	
186 FS? 01	
187 XEQ I	
188 RCL $\div$ "I1"	
189 LOG	
190 RCL $\times$ "dVBE"	
191 +	
192 RTN	
193 LBL I	Displays proper label and current.
194 FS? 02	
195 $\leftarrow$ "Imax="	
196 FC?C 02	
197 $\leftarrow$ "Imin="	
198 ARCL ST X	
199 AVIEW	
200 RTN	
201 STO 07	
202 CLX	
203 STO 04	
204 LBL 05	Increases $R_L$ by 10%.
205 1.1	
206 STO $\times$ 03	
207 GTO 00	
208 END	

## Truth Tables

---

This chapter contains two programs for testing logical expressions. The first program, “PTTBL” (*print truth table*), allows you to print a complete truth table. The second program, “ITTBL” (*interactive truth table*), allows you to display any row of a truth table.

---

## Writing a Logical Expression as a Program

Before using “PTTBL” or “ITTBL” you must enter a logical expression. This is done by writing a program that represents the expression.

Each of the storage registers  $R_{00}$  through  $R_{05}$  holds a 1 or 0. These are the inputs to the function that you write. In your program recall each register as it's needed and use the Boolean logic functions (AND, OR, and XOR) to create the expression.

Here's a simple example. This program represents the expression  $A$  OR  $B$ , where  $A$  is stored in  $R_{01}$  and  $B$  is stored in  $R_{00}$ .

```
00 < 10-Byte Prgm >
01 LBL "OR"
02 RCL 01
03 RCL 00
04 OR
05 END
```

The calculator's built-in NOT function returns the *36-bit* logical NOT of the number in the X-register. To perform a *single-bit* logical NOT, execute these three functions:

```
SIGN
LASTX
-
```

The logical expression

$$(A \text{ AND } B \text{ AND } C) \text{ OR } (A \text{ AND } \overline{B} \text{ AND } \overline{C})$$

can be represented with the following program (assuming  $A$  is in  $R_{02}$ ,  $B$  is in  $R_{01}$ , and  $C$  is in  $R_{00}$ ).

## “EXMPL” Program Listing.

### Program:

```
00 < 31-Byte Prgm >
01 LBL "EXMPL"
02 RCL 02
03 RCL 01
04 AND
05 RCL 00
06 AND
07 RCL 00
08 SIGN
09 LASTX
10 -
11 RCL 01
12 SIGN
13 LASTX
14 -
15 AND
16 RCL 02
17 AND
18 OR
19 END
```

### Comments:

Calculates  $A$  AND  $B$  AND  $C$ .  
Calculates  $\bar{C}$ .  
Calculates  $\bar{B}$ .  
Calculates  $\bar{B}$  AND  $\bar{C}$ .  
Calculates  $A$  AND  $\bar{B}$  AND  $\bar{C}$ .  
Calculates  $(A$  AND  $B$  AND  $C)$  OR  
 $(A$  AND  $\bar{B}$  AND  $\bar{C}$  )



### Note

Since the name of your program is stored in a variable (FCN), do not use a global label longer than six characters.

---

## Printing a Truth Table (“PTTBL”)

This program prints a truth table for a logical expression written as previously described. You must provide the name of the function (global label) and the number of the most significant input bit. (Bits are numbered right to left; the right-most bit is number 0 and is stored in  $R_{00}$ .)

**Required Programs.** “PTTBL” (page 141) and “FCN?” (page 156).

### Variables Used.

Description	In Program
Function name.	FCN
Loop counter.	count
Most significant bit.	msb

### Remarks.

- Registers  $R_{00}$  through  $R_{05}$  are used as input registers (bits) for the Boolean expression. Be sure to set the SIZE to at least six registers (**MODES** **▼** **SIZE** **6** **ENTER**) before running “PTTBL”.
- This program clears all of the storage registers.
- Flag 12 is used to produce double-wide output from the printer.

### Program Instructions.

1. Key the “PTTBL” and “FCN?” programs into your calculator.
2. Key in the program that represents the logical expression (described in the “Writing a Logical Expression as a Program” section on page 137).
3. Press **XEQ** **PTTBL** (to run the “PTTBL” program).
4. When you see **Function Name?**, use the ALPHA menu to type the name of the function (global label). Press **R/S**.

5. The program then prompts you for the most significant bit (msb?). Key in the number of the highest register you want to use as an input to your function ( $1 \leq \text{msb} \leq 5$ ).
6. Press **R/S** to print the truth table.

**Example.** Print a truth table for the expression on page 137. (If you haven't done it already, key in the "EXMPL" program on page 138.)

Run the "PTTBL" program.

**XEQ PTTBL**

**Function Name?**  
ABCDE FGHI JKLM NOPQ RSTUV WXYZ

Key in the name of the logical expression you want to print.

**EXMPL**

**EXMPL**  
ABCDE FGHI JKLM NOPQ RSTUV WXYZ

**R/S**

**Y: 0**  
**msb?0**

Since the logical expression uses three inputs ( $A$ ,  $B$ , and  $C$ ), the most significant bit is stored in  $R_{02}$ .

**2 R/S**

**Y: 1**  
**x: 0**

### Printer Output.

2 1 0	EXMPL
0 0 0	0
0 0 1	0
0 1 0	0
0 1 1	1
1 0 0	0
1 0 1	0
1 1 0	1
1 1 1	1

## “PTTBL” Program Listing.

### Program:

```
00 C 168-Byte Prgm
01 LBL "PTTBL"
02 XEQ "FCN?"
03 PRON
04 CF 12
05 CLST
06 ALL

07 INPUT "msb"
08 1
09 +
10 2
11 X<>Y
12 Y+X
13 1
14 -
15 1E3
16 ÷
17 STO "count"

18 CLA
19 PRA

20 RCL "msb"
21 LBL 00
22 ARCL ST X
23 " "
24 DSE ST X
25 GTO 00
26 ARCL ST X
27 " "
28 ARCL "FCN"
29 " "
30 PRA
31 SF 12
```

### Comments:

Prompts for a function name using the “FCN?” utility. Printing is enabled.

Prompts for the number of the most significant bit and sets up the loop counter.


Prints a single blank line.

Prints a table header. (Note that line 27 has seven blank spaces between the double quotes.)

32 LBL 01	Initializes the inputs (storage registers) and prepares to print a row in the truth table.
33 CLRG	
34 RCL "count"	
35 IP	
36 RCL "msb"	
37 LBL 02	Stores the input bits into the appropriate storage registers.
38 BIT?	
39 XEQ 04	
40 DSE ST X	
41 GTO 02	
42 BIT?	
43 XEQ 04	
44 XEQ IND "FCN"	Evaluates the expression for the given inputs.
45 CLA	
46 RCL "msb"	Accumulates the input bits into the Alpha register.
47 LBL 03	
48 ARCL IND ST X	
49 DSE ST X	
50 GTO 03	
51 ARCL IND ST X	Accumulates the output bit into the Alpha register. (Note that line 52 has four blank spaces between the double quotes.)
52 " "	
53 ARCL ST Y	
54 PRA	Prints a line in the truth table and completes the loop.
55 ISG "count"	
56 GTO 01	
57 CF 12	Resets the double-wide flag and ends.
58 RTN	
59 LBL 04	Stores an input bit into the storage register identified in the Y-register.
60 1	
61 STO IND ST Y	
62 R+	
63 END	
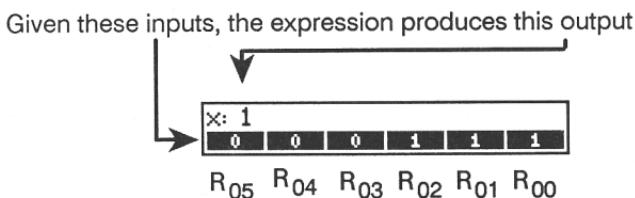
## An Interactive Truth Table (“ITTBL”)

This program allows you to change any of the inputs and display the corresponding output. Here’s a typical display:



**Required Programs.** “ITTBL” (page 145) and “FCN?” (page 156).

### Remarks.

- *FCN* (the function name) is the only variable used by this program.
- Registers R<sub>00</sub> through R<sub>05</sub> are used as input registers (bits) for the Boolean expression. Be sure to set the SIZE to at least six registers (**MODES** **▼** **SIZE 6 [ENTER]**) before running “ITTBL”.
- This program clears all of the storage registers.
- This program does not produce printed output.

### Program Instructions.

1. Key the “ITTBL” and “FCN?” programs into your calculator.
2. Key in the program that represents the logical expression (described in the “Writing a Logical Expression as a Program” section on page 137).
3. Press **[XEQ] ITTBL** (to run the “ITTBL” program).
4. When you see **Function Name?**, use the ALPHA menu to type the name of the function (global label). Press **[R/S]**.
5. The program enters an interactive mode. The menu labels represent the inputs (R<sub>05</sub> through R<sub>00</sub>) as shown above.

To change one of the inputs, press the corresponding menu key. The program returns the result to the X-register. By toggling the inputs you can view the value of the expression for any combination of inputs.

6. To quit, press **EXIT**.

**Example.** Change the inputs and view the value of the expression. (If you haven't done it already, key in the "EXMPL" program on page 138.)

Run the "ITTBL" program.

**XEQ** **ITTBL**

**Function Name?**  
ABCDE FGHI JKLM NOPQ RSTUV WXYZ

Key in the name of the logical expression you want to print. (If you just worked the example in the previous section, *FCN* probably still contains "EXMPL". Press **█**; if you see EXMPL, then simply press **R/S** to continue.)

**EXMPL**

**EXMPL\_**  
ABCDE FGHI JKLM NOPQ RSTUV WXYZ

**R/S**

**x: 0**  
0 0 0 0 0 0

Toggle the most significant bit (bit 2 for this example) by pressing the fourth menu key.

**0** (the **LOG** key)

**x: 1**  
0 0 0 1 0 0

Notice that the output (X-register) is now 1. Now toggle bits 1 and 0 (the fifth and sixth menu keys).

**0** (the **LN** key)

**x: 0**  
0 0 0 1 1 0

**0** (the **XEQ** key)

**x: 1**  
0 0 0 1 1 1

When you're finished, press **EXIT** to quit.

**EXIT**

y: 1  
x: 1

## "ITTBL" Program Listing.

### Program:

```
00 < 125-Byte Prgm >
01 LBL "ITTBL"
02 XEQ "FCN?"
03 ALENG
04 X=0?
05 GTO 09

06 BINM
07 ALL
08 CLRG
09 CLMENU

10 KEY 9 GTO 09
11 LBL A
12 CLA
13 ARCL 05
14 KEY 1 XEQ 01
15 CLA
16 ARCL 04
17 KEY 2 XEQ 02
18 CLA
19 ARCL 03
20 KEY 3 XEQ 03
21 CLA
22 ARCL 02
23 KEY 4 XEQ 04
24 CLA
25 ARCL 01
26 KEY 5 XEQ 05
27 CLA
28 ARCL 00
29 KEY 6 XEQ 06
```

### Comments:

Prompts for a function name using the "FCN?" utility.

Initializes by selecting Binary mode, selecting ALL display format, and clearing the storage registers and programmable menu definitions.

Defines the **EXIT** key to branch to LBL 09. Defines the six top-row menu keys using the numbers in the corresponding storage registers as menu labels.

30 XEQ IND "FCN"	Evaluates the logical expression and leaves the value in the X-register.
31 MENU	Displays the menu and stops.
32 STOP	Pressing <b>R/S</b> redisplays the menu.
33 GTO R	
34 LBL 01	
35 5	
36 GTO 07	Produces the appropriate register number, depending on which menu key is pressed.
37 LBL 02	
38 4	
39 GTO 07	
40 LBL 03	
41 3	
42 GTO 07	
43 LBL 04	
44 2	
45 GTO 07	
46 LBL 05	
47 1	
48 GTO 07	
49 LBL 06	
50 CLX	
51 LBL 07	
52 RCL IND ST X	Toggles the bit in a particular storage register.
53 SIGN	
54 LASTX	
55 -	
56 STO IND ST Y	
57 RTN	
58 LBL 09	Exits all menus and ends.
59 EXITALL	
60 END	

## Utilities

---

The programs in this chapter are general-purpose utilities and subroutines used by other programs in this book. You may also find them useful when writing your own programs.

---

# Circuit Calculation Utilities

## Impedance of an Element (“C→Z” and “L→Z”)

This program converts the value for a capacitor or inductor in the X-register to a complex impedance. Before executing “C→Z” (*capacitance to impedance*) or “L→Z” (*inductance to impedance*), store the radian frequency in the variable *w*.

### Remarks.

- *w* is the radian frequency,  $2\pi f$  radians/second. (A lowercase “W” is used because the HP-42S does not have a lowercase omega character.)
- This program sets Rectangular mode.

### “C→Z” and “L→Z” Program Listing.

#### Program:

```
00 C 30-Byte Prgm
01 LBL "C→Z"
02 XEQ 00
03 1/X
04 RTN
05 LBL "L→Z"
06 LBL 00
07 RECT
08 RCLX "w"
09 0
10 X<>Y
11 COMPLEX
12 END
```

#### Comments:

Calculates the impedance for the given capacitance (which is the reciprocal of impedance for inductance).

Calculates the impedance for the given inductance.

## Combining Parallel Impedances (“ZP”)

The “ZP” program takes two complex impedances (in the X- and Y-registers) and returns the combined impedance for the two elements connected in parallel.

### “ZP” Program Listing.

00 C 11-Byte Prgm	04 1/X
01 LBL "ZP"	05 +
02 1/X	06 1/X
03 X<>Y	07 END

## Entering Radian Frequency (“FQ?”)

The “FQ?” program prompts for a value of  $w$ , the radian frequency value used by several programs in this book. Whenever you see Radian Frequency( $2\pi f$ )?, key in the frequency and press **R/S**.

### Remarks.

- $w$  is the radian frequency,  $2\pi f$  radians/second. (A lowercase “W” is used because the HP-42S does not have a lowercase omega character.)
- The program sets flag 25 (*error ignore*) to prevent an error from stopping the program if  $w$  doesn’t exist.

### “FQ?” Program Listing.

00 C 44-Byte Prgm	06 RCL "w"
01 LBL "FQ?"	07 CF 25
02 "Radian Frequenc"	08 PROMPT
03 F"y(2\pi f)?"	09 STO "w"
04 SF 25	10 END
05 CLX	

---

## Circuit Element Input Utility (“EL?”)

This program displays a menu for entering six types of circuit elements. It is designed to be used by other circuit analysis programs, such as the “CIRCT” program on page 45.

Each routine in this program displays a menu for entering an element using common units. For example, when you enter a resistor, the calculator displays:



Value?  
[OHM] [KOHM] [MOHM] [S]

You can enter a 2,000-ohm resistor by pressing 2000 [OHM], 2 [KOHM], or .002 [MOHM].

The program returns two numbers to the stack:

Y: *ee.yyxx*  
X: *element value*

where the X-register contains the *element value* you keyed in adjusted to the default units shown in the following table. *ee* is the element type in the table, and *yy* and *xx* are the location numbers entered into the stack. These numbers are used by programs such as “CIRCT” to indicate where a particular element occurs in a circuit.

Element Type	Units	Type Code
Resistor	Ohms	82
Capacitor	Farads	67
Inductor	Henrys	76
General impedance	Ohms	90*
Voltage source	Volts	86*
Current source	Amperes	73*

\*If the element value is a complex number, the type code is negative.

## Remarks.

- The type code is temporarily stored in a variable named *TYPE*.
- Flag 08 is set to indicate when an element has been entered successfully.

## “EL?” Program Listing.

### Program:

```

00 < 374-Byte Prgm >
01 LBL "EL?"
02 LBL A
03 RECT
04 CF 08
05 "R"
06 KEY 1 GTO 09
07 "C"
08 KEY 2 GTO 12
09 "L"
10 KEY 3 GTO 13
11 "Z"
12 KEY 4 GTO 10
13 "V"
14 KEY 5 GTO 14
15 "I"
16 KEY 6 GTO 15
17 KEY 9 GTO 99

```

### Comments:

Defines menu for entering location and type of element. The **EXIT** key is defined to cause a branch to the “END” (which causes a return to the calling program).

```
18 "Location: "
19 ←# [ENTER] #"
20 MENU
21 PROMPT
22 GTO A

23 LBL 09
24 82
25 GTO 11

26 LBL 10
27 90

28 LBL 11
29 XEQ 00
30 "OHM"
31 KEY 1 XEQ 01
32 "KOHM"
33 KEY 2 XEQ 02
34 "MOHM"
35 KEY 3 XEQ 03
36 "S"
37 KEY 6 XEQ 08
38 GTO B

39 LBL 12
40 67
41 XEQ 00
42 "pF"
43 KEY 1 XEQ 07
44 "nF"
45 KEY 2 XEQ 06
46 "μF"
47 KEY 3 XEQ 05
48 "mF"
49 KEY 4 XEQ 04
50 "F"
51 KEY 5 XEQ 01
52 GTO B
```

Displays the input message and the menu. Pressing **R/S** redisplays the menu.

Enters the code for a resistor.

Enters the code for a general impedance.

Defines a menu for entering units for a resistor of general impedance. (The **S** in line 36 refers to the SI unit "siemens.")

Enters the code for a capacitor and defines a menu for entering units of capacitance.

```
53 LBL 13
54 76
55 XEQ 00
56 "mH"
57 KEY 1 XEQ 04
58 "H"
59 KEY 2 XEQ 01
60 "KH"
61 KEY 3 XEQ 02
62 "MH"
63 KEY 4 XEQ 03
64 GTO B

65 LBL 14
66 POLAR
67 86
68 XEQ 00
69 "mV"
70 KEY 1 XEQ 04
71 "V"
72 KEY 2 XEQ 01
73 "KV"
74 KEY 3 XEQ 02
75 GTO B

76 LBL 15
77 POLAR
78 73
79 XEQ 00
80 "mA"
81 KEY 1 XEQ 04
82 "A"
83 KEY 2 XEQ 01
84 "KA"
85 KEY 3 XEQ 02
86 GTO B
```

Enters the code for an inductor and defines a menu for entering units of inductance.

Enters the code for a voltage source and defines a menu for entering voltage units.

Enters the code for a current source and defines a menu for entering current units.

87 LBL 08  
88 1/X  
89 RTN  
90 LBL 07  
91 XEQ 04  
92 LBL 06  
93 XEQ 04  
94 LBL 05  
95 XEQ 04  
96 LBL 04  
97 1E3  
98 ÷  
99 RTN  
100 LBL 03  
101 XEQ 02  
102 LBL 02  
103 1E3  
104 ×  
105 LBL 01  
106 RTN

107 LBL 00  
108 X<>Y  
109 1  
110 %  
111 R↑  
112 +  
113 1  
114 %  
115 R↑  
116 +  
117 STO "TYPE"

118 CLMENU  
119 KEY 9 GTO A  
120 RTN

Adjusts the element value to be expressed in the *default* units.

Combines the location number and element type code into a single number and stores it in the variable **TYPE**.

Clears the programmable menu and defines the **[EXIT]** key to return to the first menu.

```
121 LBL B
122 MENU
123 1
124 "Value?"
125 PROMPT

126 SF 08
127 RCL "TYPE"
128 CLV "TYPE"
129 X<>Y
130 REAL?
131 RTN
132 X<>Y
133 +/--
134 X<>Y

135 LBL 99
136 END
```

Displays the units menu and prompts for a value. Pressing **R/S** causes the default value of 1 to be used.

Sets flag 08 to indicate an element has been entered. Returns the type code in the Y-register and the element value in the X-register. If the element value is complex, the type code is made negative.

Ends the program.

---

## Function Name Utility (“FCN?”)

This program prompts for a function name and then stores the name into a variable named *FCN*. If *FCN* contains a string, it is recalled into the Alpha register (press  $\blacktriangleleft$  to clear the Function Name? message). Use the ALPHA menu to type the name of the function (global program label) and then press **R/S** to continue.

### Remarks.

- *FCN* contains the variable name (up to six characters).
- Flag 21 (*printer enable*) is cleared by the program.
- Flag 25 (*error ignore*) is used to prevent the program from stopping if *FCN* doesn't exist.
- The plotting programs in the owner's manual use a similar technique to prompt for a function name. If you have the “FCN?” program in your calculator, you can shorten one or both of the plotting programs by calling “FCN?” as a subroutine (XEQ “FCN?”).

### “FCN?” Program Listing.

#### Program:

```
00 C 48-Byte Prgm
01 LBL "FCN?"
02 "Function Name?"
03 CF 21
04 RVIEW
05 SF 25
06 RCL "FCN"
07 CF 25
08 CLA
09 STR?
10 ARCL ST X
11 RON
12 STOP
13 AOFF
14 ASTO "FCN"
15 END
```

#### Comments:

Displays the prompt.

If *FCN* exists and contains an Alpha string, recalls that string to the Alpha register.

Turns on the ALPHA menu and stops.

Turns off the ALPHA menu and stores the first six characters in the Alpha menu into *FCN*.

---

## Yes/No Utility (“Y?N”)

This program displays a menu for a Yes/No decision. It returns a zero if you press **NO**, **R/S**, or **EXIT**; it returns a 1 if you press **YES**.

If you want to use this utility in your own programs, simply place a message in the Alpha register and then execute the utility (XEQ “Y?N”). Your program can then test the X-register to detect a “yes” (1) or a “no” (0).

### Remarks.

- Flag 21 (*printer enable*) is cleared by this program.
- This program redefines the programmable menu.

### “Y?N” Program Listing.

00 C 41-Byte Prgm )	09 KEY 9 GTO 00
01 LBL "Y?N"	10 MENU
02 CF 21	11 STOP
03 RVIEW	12 LBL 00
04 CLMENU	13 0
05 "YES"	14 RTN
06 KEY 1 GTO 01	15 LBL 01
07 "NO"	16 1
08 KEY 6 GTO 00	17 END

---

## Product Over Sum Utility (“P/S”)

This routine is quite useful for many electrical engineering applications. It simply takes two values (in the X- and Y-registers) and returns the product of the two values divided by the sum of the two values:

$$\frac{xy}{x + y}$$

**Note**

If  $x + y = 0$ , the program will error at line 05  
(Divide by 0).

---

### “P/S” Program Listing.

```
00 < 15-Byte Prgm >
01 LBL "P/S"
02 RCLX ST Y
03 X<>Y
04 RCL+ ST L
05 ÷
06 END
```

---

## Size Utility (“SIZE?”)

This program returns the number of storage registers available.

### “SIZE?” Program Listing.

00 < 27-Byte Prgm >	06 FC?C 25
01 LBL "SIZE?"	07 RTN
02 SF 25	08 DIM?
03 RCL "REGS"	09 X
04 FC? 25	10 END
05 0	

# *Step-by-Step Solutions for Your HP-42S Calculator*

---

*Electrical Engineering* contains a variety of programs and examples to provide solutions for electrical engineers and engineering students.

## ■ **Circuit Calculations**

Voltage Division • Current Division • Power Triangle • Frequency Response of Transfer Function • RC Timing • Delta-Wye Conversions

## ■ **Network Analysis**

Using the Circuit Editor • Mesh Analysis • Nodal Analysis  
• Impedance of a Ladder Network

## ■ **Filter Design**

Active Filter Design • Butterworth Filter Design

## ■ **Transmission Lines**

Transmission Line Calculations • Transmission Line Impedance

## ■ **Amplifier Analysis**

Transistor Amplifier Performance • Transistor Amplifier Bias Optimization

## ■ **Truth Tables**

Writing a Logical Expression as a Program • Printing a Truth Table  
• An Interactive Truth Table

## ■ **Utilities**

Circuit Calculation Utilities • Circuit Element Input Utility • Function Name Utility • Yes/No Utility • Product Over Sum Utility • Size Utility

**Reorder Number****00042-90021**00042-90023 English  
Printed in Canada 11/88

Scan Copyright ©  
The Museum of HP Calculators  
[www.hpmuseum.org](http://www.hpmuseum.org)

Original content used with permission.

Thank you for supporting the Museum of HP  
Calculators by purchasing this Scan!

Please do not make copies of this scan or  
make it available on file sharing services.